

ASSIGNMENT 1 : COMBINATIONAL CIRCUITS

Instructions: Please download, print, provide answers using the spaces provided, scan and submit on vclass before or on the due date.

QUESTION

(1) Draw the truth table for a full subtractor.

(2) Implement a full subtractor using an appropriate multiplexer.