

## **PRACTICE TEST**

### **Semiconductor Basics**

**1.** The outermost orbit of an atom can have a maximum of ..... electrons.

- (i) 8 (ii) 6  
(iii) 4 (iv) 3

**2.** When the outermost orbit of an atom has less than 4 electrons, the material is generally a .....

- (i) non-metal (ii) metal  
(iii) semiconductor (iv) none of above

**3.** The valence electrons have.....

- (i) very small energy  
(ii) least energy  
(iii) maximum energy  
(iv) none of the above

**4.** A large number of free electrons exist in .....

- (i) semiconductors (ii) metals  
(iii) insulators (iv) non-metals

**5.** An ideal voltage source has ..... internal resistance.

- (i) small (ii) large  
(iii) infinite (iv) zero

**6.** An ideal current source has ..... internal resistance.

- (i) infinite (ii) zero  
(iii) small (iv) none of the above

**7.** Maximum power is transferred if load resistance is equal to ..... of the source.

- (i) half the internal resistance  
(ii) internal resistance  
(iii) twice the internal resistance  
(iv) none of the above

**8.** Efficiency at maximum power transfer is .....

- (i) 75% (ii) 25%  
(iii) 90% (iv) 50%

**9.** When the outermost orbit of an atom has exactly 4 valence electrons, the material is generally .....

- (i) a metal (ii) a non-metal  
(iii) a semiconductor  
(iv) an insulator

**10.** Thevenin's theorem replaces a complicated circuit facing a load by an.....

- (i) ideal voltage source and parallel resistor  
(ii) ideal current source and parallel resistor  
(iii) ideal current source and series resistor  
(iv) ideal voltage source and series resistor

**11.** The output voltage of an ideal voltage source is .....

- (i) zero (ii) constant  
(iii) dependent on load resistance  
(iv) dependent on internal resistance

**12.** The current output of an ideal current source is .....

- (i) zero (ii) constant  
(iii) dependent on load resistance  
(iv) dependent on internal resistance

**13.** Norton's theorem replaces a complicated circuit facing a load by an .....

- (i) ideal voltage source and parallel resistor  
(ii) ideal current source and parallel resistor  
(iii) ideal voltage source and series resistor  
(iv) ideal current source and series resistor

**14.** The practical example of ideal voltage source is .....

- (i) lead-acid cell (ii) dry cell  
(iii) Daniel cell (iv) none of the above

**15.** The speed of electrons in vacuum is ..... than in a conductor.

- (i) less (ii) much more  
(iii) much less (iv) none of the above

**16.** Maximum power will be transferred from a source of  $10\ \Omega$  resistance to a load of

.....

- (i)  $5\ \Omega$  (ii)  $20\ \Omega$
- (iii)  $10\ \Omega$  (iv)  $40\ \Omega$

**17.** When the outermost orbit of an atom has more than 4 electrons, the material is generally a .....

- (i) metal (ii) non-metal
- (iii) semiconductor (iv) none of the above

**18.** An ideal source consists of 5 V in series with  $10\ \text{k}\Omega$  resistance. The current magnitude of equivalent current source is

.....

- (i) 2 mA (ii) 3.5 mA
- (iii) 0.5 mA (iv) none of the above

**19.** To get Thevenin voltage, you have to

.....

- (i) short the load resistor
- (ii) open the load resistor
- (iii) short the voltage source
- (iv) open the voltage source

**20.** To get the Norton current, you have to

.....

- (i) short the load resistor
- (ii) open the load resistor
- (iii) short the voltage source
- (iv) open the voltage source

**21.** The open-circuited voltage at the terminals of load  $R$  in a network is 30 V. Under the conditions of maximum power transfer, the load voltage will be ..... $L$

- (i) 30 V (ii) 10 V
- (iii) 5 V (iv) 15 V

**22.** Under the conditions of maximum power transfer, a voltage source is delivering a power of 30 W to the load. The power produced by the source is .....

- (i) 45 W (ii) 60 W
- (iii) 30 W (iv) 90 W

**23.** The maximum power transfer theorem is used in .....

- (i) electronic circuits
- (ii) power system
- (iii) home lighting circuits
- (iv) none of the above

**24.** The Norton resistance of a network is  $20\ \Omega$  and the shorted-load current is 2 A. If the network is loaded by a resistance equal to  $20\ \Omega$ , the current through the load will be

.....

- (i) 2 A (ii) 0.5 A
- (iii) 4 A (iv) 1 A

**25.** The Norton current is sometimes called the.....

- (i) shorted-load current
- (ii) open-load current
- (iii) Thevenin current
- (iv) Thevenin voltage

## **PN Junction Diode**

**1.** A semiconductor is formed by..... bonds.

- (i) covalent (ii) electrovalent
- (iii) co-ordinate (iv) none of the above

**2.** A semiconductor has ..... temperature coefficient of resistance.

- (i) positive (ii) zero
- (iii) negative (iv) none of the above

**3.** The most commonly used semiconductor is.....

- (i) germanium (ii) silicon
- (iii) carbon (iv) sulphur

**4.** A semiconductor has generally..... valence electrons.

- (i)2 (ii)3
- (iii)6 (iv)4

**5.** The resistivity of pure germanium under standard conditions is about .....

- (i)  $6 * 10^4 \Omega \text{ cm}$  (ii)  $60 \Omega \text{ cm}$
- (iii)  $3 * 10^6 \text{ cm}$  (iv)  $6 * 10^{-4} \Omega \text{ cm}$

**6.** The resistivity of pure silicon is about .....

- (i)  $100 \Omega \text{ cm}$  (ii)  $6000 \Omega \text{ cm}$
- (iii)  $3 * 10^5 \Omega \text{ cm}$  (iv)  $1.6 * 10^{-8} \Omega \text{ cm}$

**7.** When a pure semiconductor is heated, its resistance .....

- (i) goes up (ii) goes down
- (iii) remains the same (iv) cannot say

**8.** The strength of a semiconductor crystal comes from .....

- (i) forces between nuclei
- (ii) forces between protons
- (iii) electron-pair bonds
- (iv) none of the above

**9.** When a pentavalent impurity is added to a pure semiconductor, it becomes .....

- (i) an insulator
- (ii) an intrinsic semiconductor
- (iii) *p*-type semiconductor
- (iv) *n*-type semiconductor

**10.** Addition of pentavalent impurity to a semi-conductor creates many.....

- (i) free electrons (ii) holes
- (iii) valence electrons
- (iv) bound electrons

**11.** A pentavalent impurity has..... valence electrons.

- (i)3 (ii)5
- (iii)4 (iv)6

**12.** An *n*-type semiconductor is.....

- (i) positively charged
- (ii) negatively charged
- (iii) electrically neutral
- (iv) none of the above

**13.** A trivalent impurity has..... valence electrons.

- (i)4 (ii)5
- (iii)6 (iv)3

**14.** Addition of trivalent impurity to a semiconductor creates many .....

- (i) holes (ii) free electrons
- (iii) valence electrons
- (iv) bound electrons

**15.** A hole in a semiconductor is defined as .....

- (i) a free electron
- (ii) the incomplete part of an electron pair bond
- (iii) a free proton
- (iv) a free neutron

**16.** The impurity level in an extrinsic semiconductor is about ..... of pure semiconductor.

- (i) 10 atoms for  $10^8$  atoms
- (ii) 1 atom for  $10^8$  atoms

- (iii) 1 atom for  $10^4$  atoms
- (iv) 1 atom for 100 atoms

**17.** As the doping to a pure semiconductor increases, the bulk resistance of the semiconductor .....

- (i) remains the same
- (ii) increases
- (iii) decreases
- (iv) none of the above

**18.** A hole and electron in close proximity would tend to .....

- (i) repel each other
- (ii) attract each other
- (iii) have no effect on each other
- (iv) none of the above

**19.** In a semiconductor, current conduction is due .....

- (i) only to holes
- (ii) only to free electrons
- (iii) to holes and free electrons
- (iv) none of the above

**20.** The random motion of holes and free electrons due to thermal agitation is called.....

- (i) diffusion (ii) pressure
- (iii) ionisation (iv) none of the above

**21.** A forward biased *pn* junction has a resistance of the.....

- (i) order of  $\Omega$  (ii) order of  $k \Omega$
- (iii) order of  $M \Omega$  (iv) none of the above

**22.** The battery connections required to forward bias a *pn* junction are .....

- (i) +ve terminal to *p* and -ve terminal to *n*
- (ii) -ve terminal to *p* and +ve terminal to *n*
- (iii) -ve terminal to *p* and -ve terminal to *n*
- (iv) none of the above

**23.** The barrier voltage at a *pn* junction for germanium is about .....

- (i) 3.5 V (ii) 3V

- (iii) zero (iv) 0.3 V

**24.** In the depletion region of a *pn* junction, there is a shortage of .....

- (i) acceptor ions (ii) holes and electrons
- (iii) donor ions (iv) none of the above

**25.** A reverse biased *pn* junction has .....

- (i) very narrow depletion layer
- (ii) almost no current
- (iii) very low resistance
- (iv) large current flow

**26.** A *pn* junction acts as a .....

- (i) controlled switch
- (ii) bidirectional switch
- (iii) unidirectional switch
- (iv) none of the above

**27.** A reverse biased *pn* junction has resistance of the.....

- (i) order of  $\Omega$  (ii) order of  $k \Omega$
- (iii) order of  $M \Omega$  (iv) none of the above

**28.** The leakage current across a *pn* junction is due to .....

- (i) minority carriers
- (ii) majority carriers
- (iii) junction capacitance
- (iv) none of the above

**29.** When the temperature of an extrinsic semiconductor is increased, the pronounced Effect is on .....

- (i) junction capacitance
- (ii) minority carriers
- (iii) majority carriers
- (iv) none of the above

**30.** With forward bias to a *pn* junction, the width of depletion layer.....

- (i) decreases (ii) increases
- (iii) remains the same
- (iv) none of the above

**31.** The leakage current in a *pn* junction is of the order of .....

- (i) A (ii) mA
- (iii) kA (iv)  $\mu$ A

**32.** In an intrinsic semiconductor, the number of free electrons .....

- (i) equals the number of holes
- (ii) is greater than the number of holes
- (iii) is less than the number of holes
- (iv) none of the above

(iii) many free electrons

(iv) no holes or free electrons

**35.** At room temperature, an intrinsic silicon crystal acts approximately as .....

- (i) a battery
- (ii) a conductor
- (iii) an insulator
- (iv) a piece of copper wire

**33.** At room temperature, an intrinsic semiconductor has .....

- (i) many holes only
- (ii) a few free electrons and holes
- (iii) many free electrons only
- (iv) no holes or free electrons

**34.** At absolute temperature, an intrinsic semiconductor has .....

- (i) a few free electrons
- (ii) many holes

## **PN Junction Diode Application**

**1.** A crystal diode has.....

- (i) one *pn* junction
- (ii) two *pn* junctions
- (iii) three *pn* junctions
- (iv) none of the above

**2.** A crystal diode has forward resistance of the order of .....

- (i)  $k\Omega$  (ii)  $\Omega$
- (iii)  $M\Omega$  (iv) none of the above

**3.** If the arrow of crystal diode symbol is positive w.r.t. bar, then diode is..... biased.

- (i) forward
- (ii) reverse
- (iii) either forward or reverse
- (iv) none of the above

**4.** The reverse current in a diode is of the order of .....

- (i) kA (ii) mA
- (iii)  $\mu A$  (iv) A

**5.** The forward voltage drop across a silicon diode is about .....

- (i) 2.5 V (ii) 3 V
- (iii) 10 V (iv) 0.7 V

**6.** A crystal diode is used as .....

- (i) an amplifier (ii) a rectifier
- (iii) an oscillator (iv) a voltage regulator

**7.** The d.c. resistance of a crystal diode is .....its a.c. resistance.

- (i) the same as (ii) more than
- (iii) less than (iv) none of the above

**8.** An ideal crystal diode is one which behaves as a perfect ..... when forward biased.

- (i) conductor
- (ii) insulator
- (iii) resistance material
- (iv) none of the above

**9.** The ratio of reverse resistance and forward resistance of a germanium crystal diode is about .....

- (i) 1 : 1 (ii) 100 : 1
- (iii) 1000 : 1 (iv) 40000 : 1

**10.** The leakage current in a crystal diode is due to .....

- (i) minority carriers
- (ii) majority carriers
- (iii) junction capacitance
- (iv) none of the above

**11.** If the temperature of a crystal diode increases, then leakage current .....

- (i) remains the same
- (ii) decreases
- (iii) increases
- (iv) becomes zero

**12.** The PIV rating of a crystal diode is ..... that of equivalent vacuum diode.

- (i) the same as (ii) lower than
- (iii) more than (iv) none of the above

**13.** If the doping level of a crystal diode is increased, the breakdown voltage .....

- (i) remains the same
- (ii) is increased
- (iii) is decreased
- (iv) none of the above

**14.** The knee voltage of a crystal diode is approximately equal to .....

- (i) applied voltage
- (ii) breakdown voltage
- (iii) forward voltage
- (iv) barrier potential

**15.** When the graph between current through and voltage across a device is a straight line, the device is referred to as .....

- (i) linear (ii) active
- (iii) nonlinear (iv) passive

**16.** When the crystal diode current is large, the bias is .....

- (i) forward (ii) inverse
- (iii) poor (iv) reverse

**17.** A crystal diode is a ..... device.

- (i) non-linear (ii) bilateral
- (iii) linear (iv) none of the above

**18.** A crystal diode utilises ..... characteristic for rectification.

- (i) reverse (ii) forward
- (iii) forward or reverse
- (iv) none of the above

**19.** When a crystal diode is used as a rectifier, the most important consideration is .....

- (i) forward characteristic
- (ii) doping level
- (iii) reverse characteristic
- (iv) PIV rating

**20.** If the doping level in a crystal diode is increased, the width of depletion layer .....

- (i) remains the same
- (ii) is decreased
- (iii) is increased
- (iv) none of the above

**21.** A zener diode has .....

- (i) one *pn* junction
- (ii) two *pn* junctions
- (iii) three *pn* junctions
- (iv) none of the above

**22.** A zener diode is used as .....

- (i) an amplifier (ii) a voltage regulator
- (iii) a rectifier (iv) a multivibrator

**23.** The doping level in a zener diode is ..... that of a crystal diode.

- (i) the same as (ii) less than
- (iii) more than (iv) none of the above

**24.** A zener diode is always ..... connected.

- (i) reverse
- (ii) forward
- (iii) either reverse or forward
- (iv) none of the above

**25.** A zener diode utilises ..... characteristic for its operation.

- (i) forward
- (ii) reverse
- (iii) both forward and reverse
- (iv) none of the above

**26.** In the breakdown region, a zener diode behaves like a ..... source.

- (i) constant voltage
- (ii) constant current
- (iii) constant resistance
- (iv) none of the above

**27.** A zener diode is destroyed if it .....

- (i) is forward biased
- (ii) is reverse biased
- (iii) carries more than rated current
- (iv) none of the above

**28.** A series resistance is connected in the Zener circuit to .....

- (i) properly reverse bias the zener
- (ii) protect the zener
- (iii) properly forward bias the zener
- (iv) none of the above

**29.** A zener diode is ..... device.

- (i) a non-linear (ii) a linear
- (iii) an amplifying (iv) none of the above

**30.** A zener diode has ..... breakdown voltage.

- (i) undefined (ii) sharp
- (iii) zero (iv) none of the above

**31.** ..... rectifier has the lowest forward resistance.

- (i) solid state (ii) vacuum tube

(iii) gas tube (iv) none of the above

**32.** Mains a.c. power is converted into d.c. power for .....

- (i) lighting purposes
- (ii) heaters
- (iii) using in electronic equipment
- (iv) none of the above

**33.** The disadvantage of a half-wave rectifier is that the .....

- (i) components are expensive
- (ii) diodes must have a higher power rating
- (iii) output is difficult to filter
- (iv) none of the above

**34.** If the a.c. input to a half-wave rectifier has an r.m.s. value of  $400/\sqrt{2}$  volts, then diode PIV rating is .....

- (i)  $400/\sqrt{2}$  V (ii) 400 V
- (iii)  $400 * \sqrt{2}$  V (iv) none of the above

**35.** The ripple factor of a half-wave rectifier is.....

- (i) 2 (ii) 1.21
- (iii) 2.5 (iv) 0.48

**36.** There is a need of transformer for .....

- (i) half-wave rectifier
- (ii) centre-tap full-wave rectifier
- (iii) bridge full-wave rectifier
- (iv) none of the above

**37.** The PIV rating of each diode in a bridge rectifier is ..... that of the equivalent centretap rectifier.

- (i) one-half (ii) the same as
- (iii) twice (iv) four times

**38.** For the same secondary voltage, the output voltage from a centre-tap rectifier is .....than that of bridge rectifier.

- (i) twice (ii) thrice
- (iii) four times (iv) one-half

**39.** If the PIV rating of a diode is exceeded,.....

- (i) the diode conducts poorly
- (ii) the diode is destroyed
- (iii) the diode behaves as zener diode
- (iv) none of the above

**40.** A 10 V power supply would use ..... as filter capacitor.

- (i) paper capacitor (ii) mica capacitor
- (iii) electrolytic capacitor
- (iv) air capacitor

**41.** A 1000 V power supply would use ..... as a filter capacitor.

- (i) paper capacitor
- (ii) air capacitor
- (iii) mica capacitor
- (iv) electrolytic capacitor

**42.** The ..... filter circuit results in the best voltage regulation.

- (i) choke input
- (ii) capacitor input
- (iii) resistance input
- (iv) none of the above

**43.** A half-wave rectifier has an input voltage of 240 V r.m.s. If the step-down transformer has a turns ratio of 8 : 1, what is the peak load voltage ? Ignore diode drop.

- (i) 27.5 V (ii) 86.5 V
- (iii) 30 V (iv) 42.5 V

**44.** The maximum efficiency of a half-wave rectifier is .....

- (i) 40.6% (ii) 81.2%
- (iii) 50% (iv) 25%


**45.** The most widely used rectifier is .....

- (i) half-wave rectifier
- (ii) centre-tap full-wave rectifier
- (iii) bridge full-wave rectifier
- (iv) none of the above



## THEORY

1. What is wrong the diode?

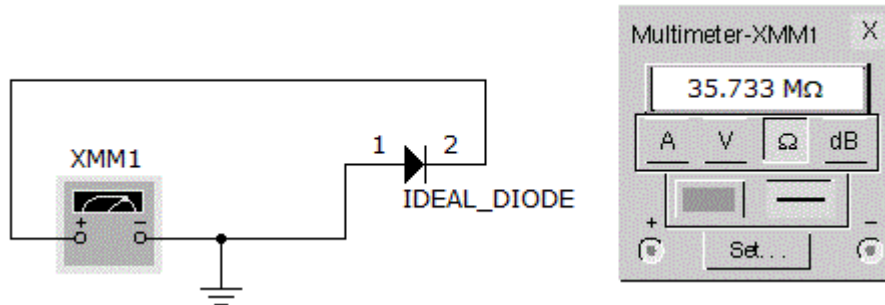

- Open
  - Short
  - Nothing
  - Not enough data
2. If a 169.7 V half-wave peak has an average voltage of 54 V, what is the average of two full-wave peaks?
3. A half-wave rectifier has a load resistance of 3.5 KΩ. If the diode and secondary of the transformer have a total resistance of 800KΩ and the ac input voltage has 240 V (peak value), determine:
- Peak, rms and average values of current through load
  - DC power output
  - AC power input
  - Rectification efficiency
4. A full wave bridge rectifier is fed with a voltage,  $50 \sin 100 \pi t$ . Its load resistance is 400Ω. The diodes used in the rectifier have an average forward resistance of 30Ω. Compute the
- Average and rms values of load current,
  - Ripple factor
  - Efficiency of rectification.
5. The zener diode in the circuit shown below regulates at 50V, over a range of diode currents from 5mA to 40mA. The supply voltage  $V = 150V$ . Compute the value of R to allow voltage regulation from a zero load current to a maximum load current  $I_{Lmax}$ . What is  $I_{Lmax}$ ?

