



# EE/COE 152: Basic Electronics

## Lecture 4

Andrew Selasi Agbemenu




## Outline

- Filter Design
- Zener Diodes
- Diode Small-signal Analysis




## Diodes Recap: A Diode Puzzle

Which lamps will light up?

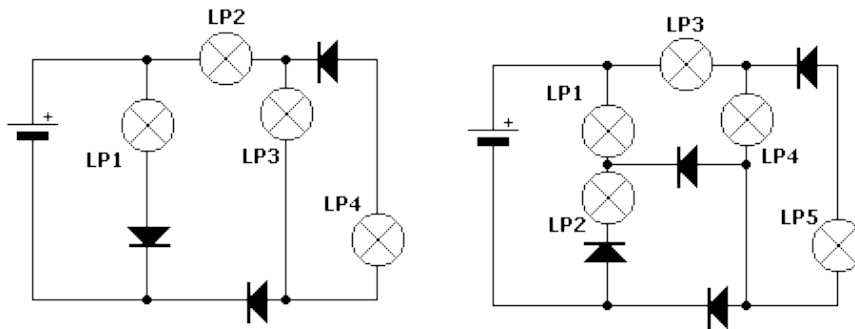



## A Diode Puzzle

Which lamps will light up?

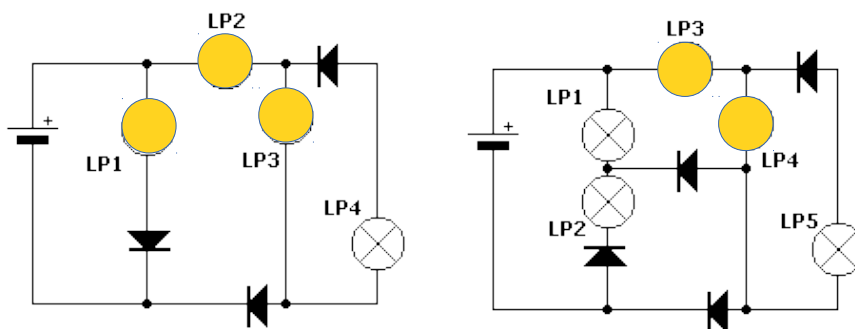




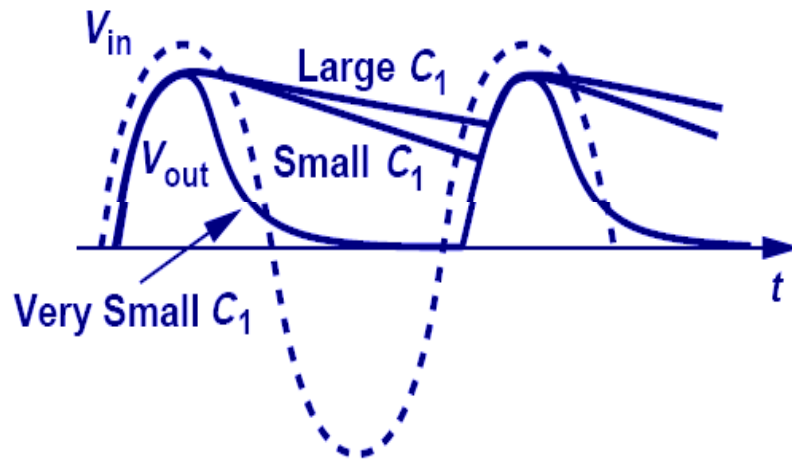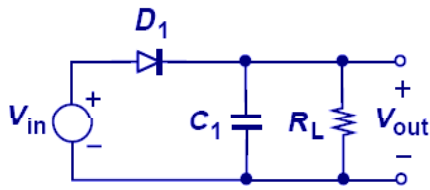
## Effect of Filter Capacitor Values on Rectifier Circuits


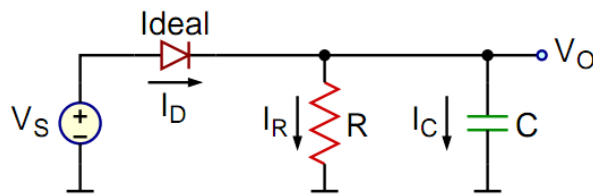
## Half-Wave Rectifier with a Filter Capacitor



$V_r$  is the **Ripple Voltage**

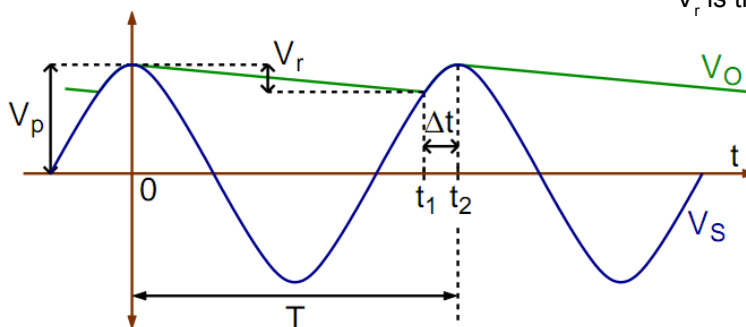


$$V_0(t) = \begin{cases} V_s(t), & t_1 < t < t_2 \\ V_p e^{-\frac{t}{RC}}, & 0 < t < t_1 \end{cases} \Rightarrow V_0(t_1) = V_p e^{-\frac{t_1}{RC}}$$


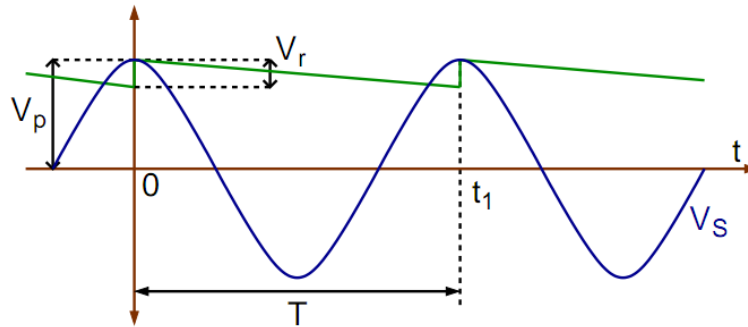
## Half-Wave Rectifier with a Filter Capacitor

For minimum ripple effect:  $t_1 \approx T$ , the period



$$V_o(t_1) \approx V_p e^{-\frac{T}{RC}}$$

$$\text{for } RC \gg T \Rightarrow e^{-\frac{T}{RC}} \approx 1 - \frac{T}{RC}$$

Peak-to-peak ripple voltage:

$$V_r = V_p - V_o(t_1) = V_p - V_p \left(1 - \frac{T}{RC}\right) \Rightarrow V_r = V_p \frac{T}{RC}$$



## Exercise: Rectifier with a Filter Capacitor

Half-wave rectifier peak-to-peak ripple voltage ratio:

$$V_r(\text{ratio}) = \frac{V_r}{V_p} = \frac{T}{RC}$$

Exercise:

Show that the peak-to-peak ripple voltage ratio of a full-wave Rectifier is half that of a half-wave rectifier





# Zener Diodes

- Diodes in their normal operation will get destroyed when breakdown in the reverse bias mode
- Zener diode is a type of diode that can operate normally above the breakdown voltage (**Zener voltage**)
- They are normally used as Voltage regulators
- Zener diode will maintain a constant reverse bias voltage ( $V_Z$ ) and limit the zener current ( $I_Z$ ) passes through




# Zener Diode Characteristics

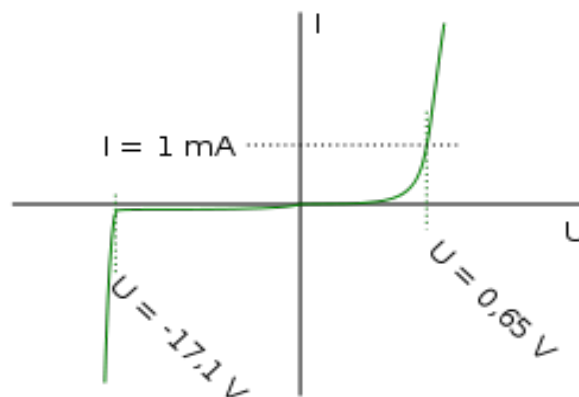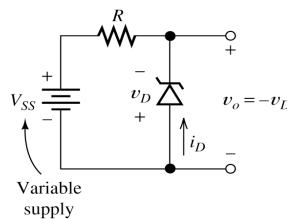




## Zener Diode Model

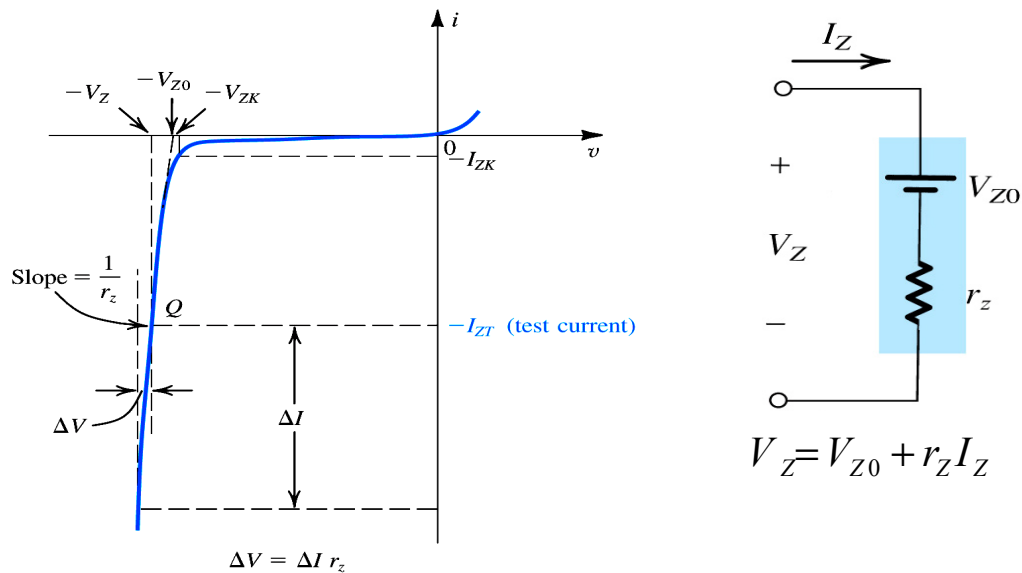

## Zener Diode Regulator

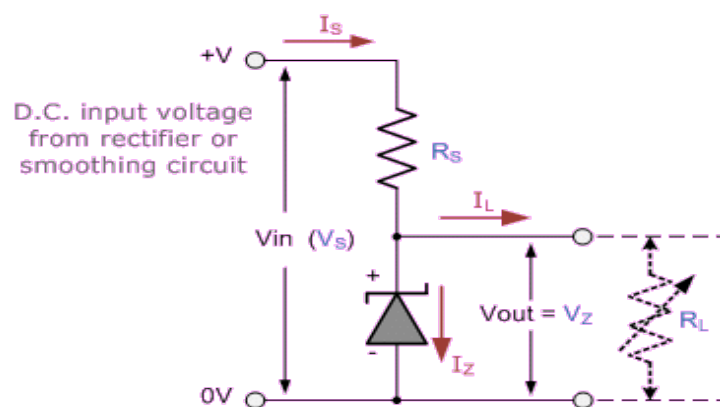

$R_S$  is used to limit the amount of current that flows through the Zener diode to  $I_Z$ . This allows a constant voltage drop of  $V_Z$  across the diode and hence the load.




## Some Typical Zener Diode Standard Voltages

BZX55 Zener Diode Power Rating 500mW							
2.4V	2.7V	3.0V	3.3V	3.6V	3.9V	4.3V	4.7V
5.1V	5.6V	6.2V	6.8V	7.5V	8.2V	9.1V	10V
11V	12V	13V	15V	16V	18V	20V	22V
24V	27V	30V	33V	36V	39V	43V	47V

BZX85 Zener Diode Power Rating 1.3W							
3.3V	3.6V	3.9V	4.3V	4.7V	5.1V	5.6	6.2V
6.8V	7.5V	8.2V	9.1V	10V	11V	12V	13V
15V	16V	18V	20V	22V	24V	27V	30V
33V	36V	39V	43V	47V	51V	56V	62V



## Example: Zener Diode Regulator

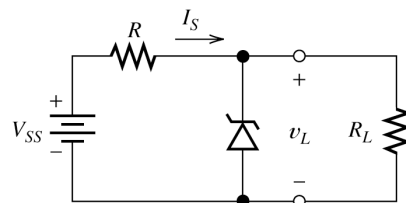

(a) Regulator circuit with load


Consider the Zener diode regulator shown in (a) above.  
Find the load voltage,  $v_L$  and the source current  $i_s$  if

$V_{ss} = 24V$ ,  $R = 1.2k\Omega$  and  $R_L = 6k\Omega$



# Solution

First find the Thevenin equivalent circuit

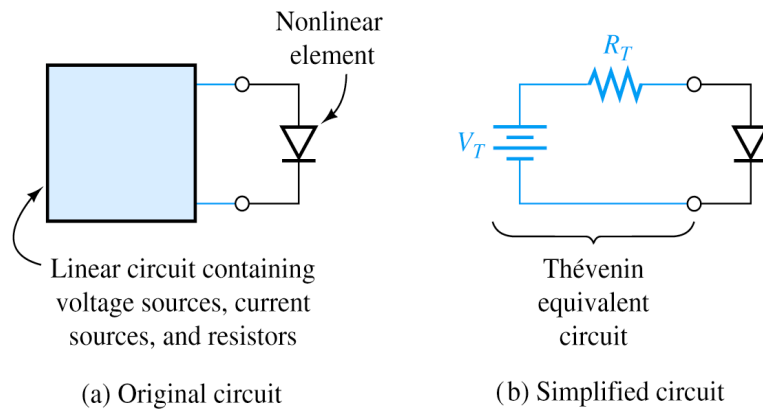

**Figure 10.11** Analysis of a circuit containing a single nonlinear element can be accomplished by load-line analysis of a simplified circuit.



# Solution


*Thevenin equivalent*

$$V_T = V_{ss} \frac{R_L}{R + R_L} = 20V$$

$$R_T = \frac{RR_L}{R + R_L} = 1k\Omega$$

*Load Line Equation*

$$V_T + R_T i_D + V_D = 0$$

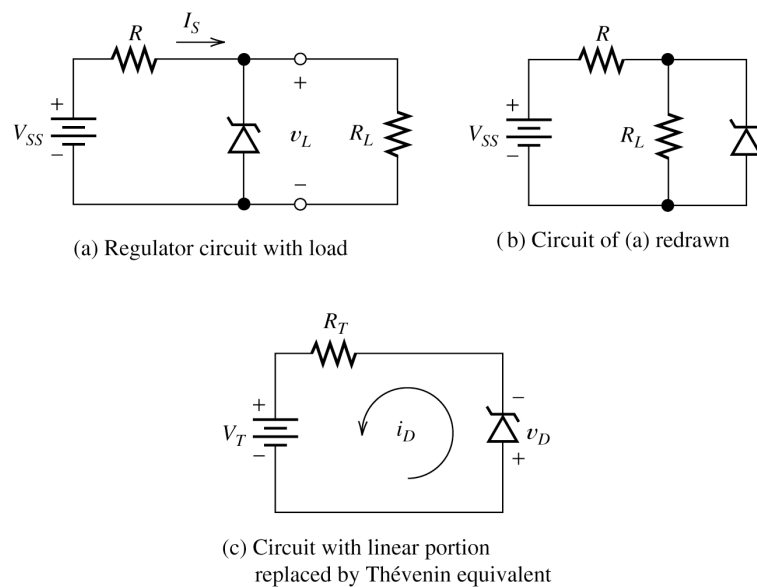





## Solution

Plot load line on  
Zener diode characteristic  
Curve.

Determine  $V_D$  and  $i_D$   
From the Q-point

*From Graph*

$$V_i = -V_D = 10V$$

$$i_D = -10mA$$

Now find  $i_S$


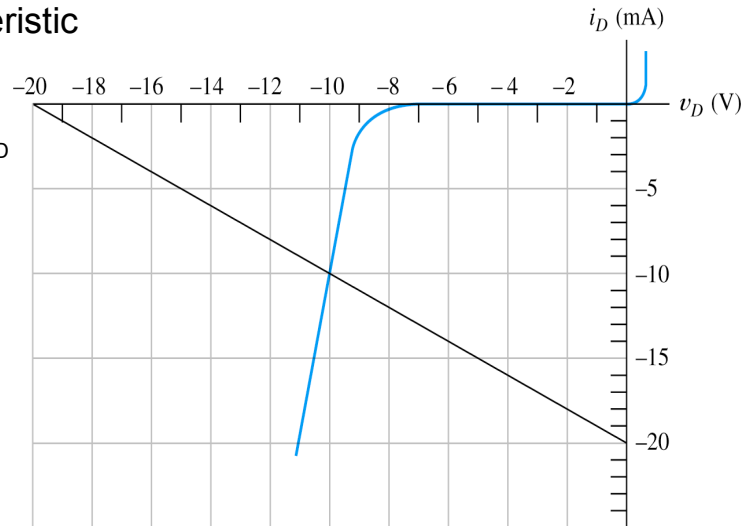


Figure 10.13 Zener-diode characteristic for Example 10.4 and Exercise 10.4.

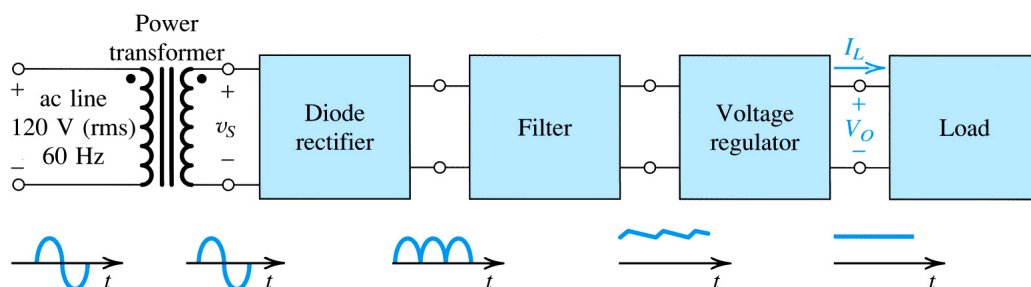


At this point you should be able to design a DC power supply  
With all the Blocks shown below





## Diode Small Signal Model

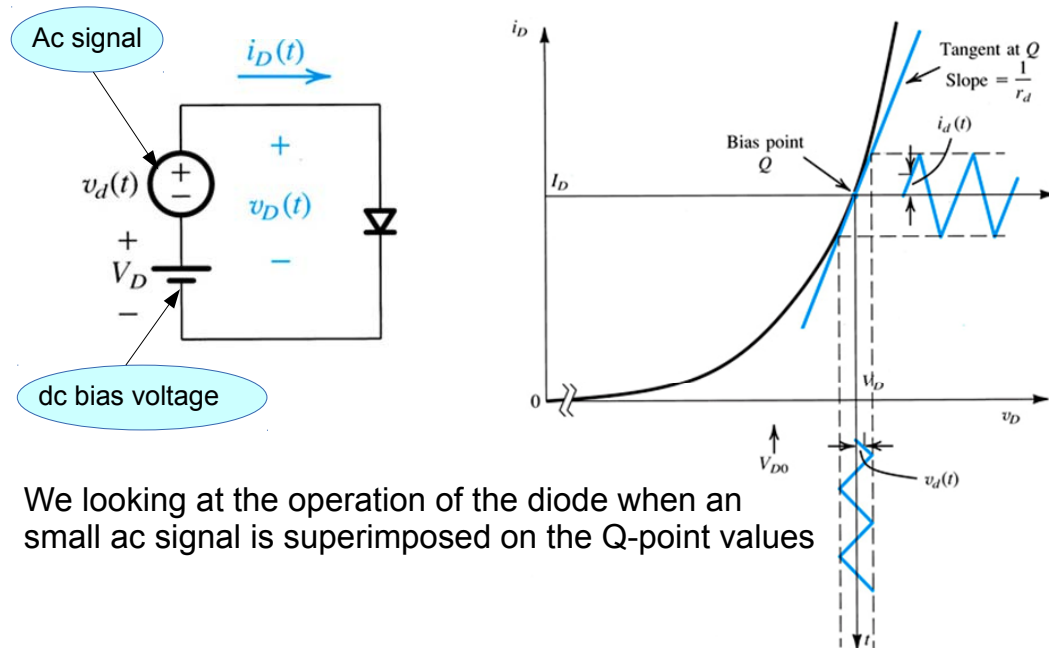

We looking at the operation of the diode when an small ac signal is superimposed on the Q-point values



## Small-signal Approximation

*Using KVL*

$$v_d(t) = V_D + v_d(t)$$

*Using Shockley (Diode) Equation:*


$$i_D(t) = I_s e^{\frac{v_D(t)}{nV_T}} = I_s e^{\frac{V_D}{nV_T}} e^{\frac{v_d(t)}{nV_T}} = I_D e^{\frac{v_d}{nV_T}}$$

where  $V_D, I_D$  are the Q-point values

under small-signal condition:  $\frac{v_d}{nV_T} \ll 1$

$$i_d(t) \approx I_D \left(1 + \frac{v_d}{nV_T}\right) = I_D + i_d$$

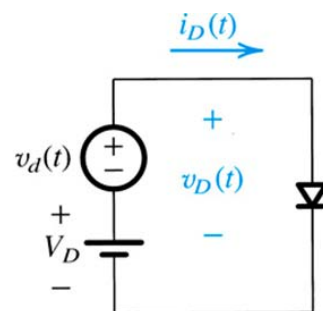Small-signal resistance:  $r_d = \frac{I_D}{nV_T}$






# Small-Signal Circuit Analysis

- Choose proper dc analysis technique or model to obtain Q-point by elimination all ac sources
- Calculate small signal parameters ( $r_d$ )
- Eliminate DC sources, replace diode with its small signal equivalent model ( $r_d$ )



## Example

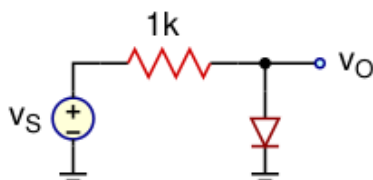

$$v_S = 5 + 0.2 \sin(\omega t), \quad n = 2$$

Find  $v_O(t)$ .

**DC Solution:**

$$V_O = 0.7 \text{ V} \quad I_D = \frac{5 - 0.7}{1\text{k}} = 4.3 \text{ mA}$$

$$r_d = \frac{nV_T}{I_D} = \frac{50 \text{ mV}}{4.3 \text{ mA}} = 11.6 \Omega$$

**AC Solution:**

$$v_o(t) = \frac{11.6}{10^3 + 11.6} 0.2 \sin(\omega t) = 2.3 \times 10^{-3} \sin(\omega t)$$

$$\text{Total: } v_O(t) = V_O + v_o(t) = 0.7 + 2.3 \times 10^{-3} \sin(\omega t)$$

