

## **Lecture 13 - Digital Circuits (II)**

### **MOS INVERTER CIRCUITS**

March 20, 2003

#### **Contents:**

1. NMOS inverter with resistor pull-up (cont.)
2. NMOS inverter with current-source pull-up
3. Complementary MOS (CMOS) Inverter



#### **Reading assignment:**

Howe and Sodini, Ch. 5, §5.3

## Key questions

- What are the key design trade-offs of the NMOS inverter with resistor pull-up?
- How can one improve upon these trade-offs?
- What is special about a CMOS inverter?
  
# 1. NMOS inverter with resistor pull-up (*cont.*)




□ Noise margins:

$$NM_L = V_{IL} - V_{OL} = V_M - \frac{V_{MAX} - V_M}{|A_v(V_M)|} - V_{MIN}$$

$$NM_H = V_{OH} - V_{IH} = V_{MAX} - V_M \left( 1 + \frac{1}{|A_v(V_M)|} \right) - \frac{V_{MIN}}{|A_v(V_M)|}$$

Need to compute  $|A_v(V_M)|$ .

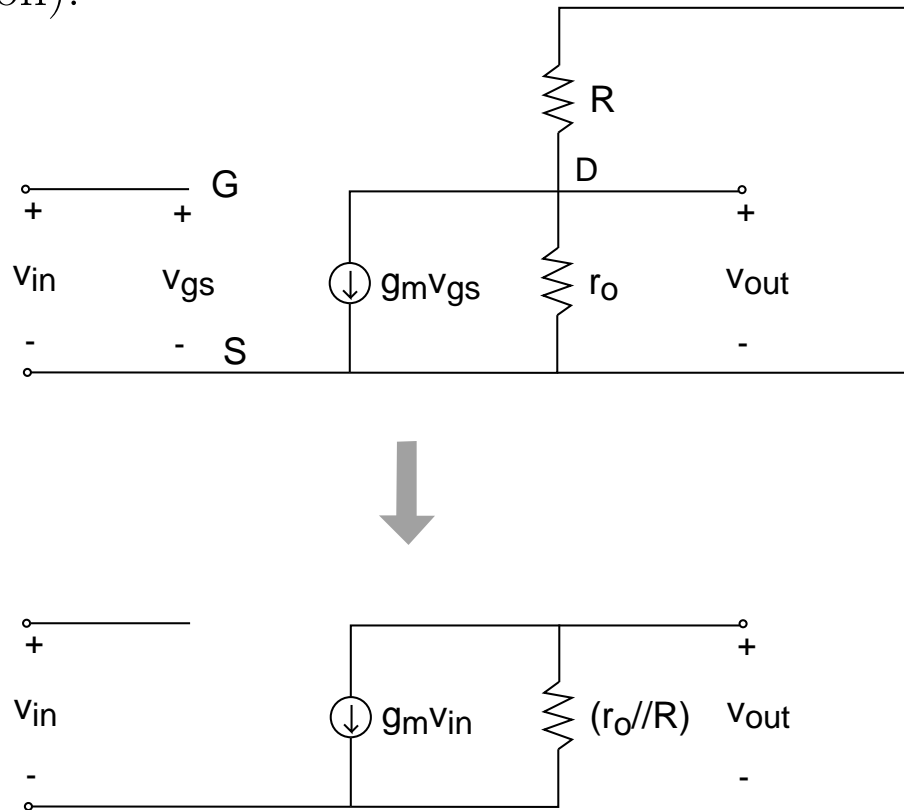Small-signal equivalent circuit model at  $V_M$  (transistor in saturation):



$$v_{out} = -g_m v_{in} (r_o // R)$$

Then:

$$A_v = \frac{v_{out}}{v_{in}} = -g_m (r_o // R) \simeq -g_m R$$



Then:

$$|A_v(V_M)| = g_m(V_M) R$$

From here, get  $NM_L$  and  $NM_H$  using above formulae.
  
## □ Dynamics

- $C_L$  *pull-down* limited by current through transistor [will study in detail with CMOS]
- $C_L$  *pull-up* limited by resistor ( $t_{PLH} \sim RC_L$ )
- pull-up slowest



□ Inverter design issues:

noise margins  $\uparrow \Rightarrow |A_v| \uparrow \Rightarrow$

- $R \uparrow \Rightarrow RC_L \uparrow \Rightarrow$  slow switching
- $g_m \uparrow \Rightarrow W \uparrow \Rightarrow$  big transistor  
(slow switching at input)

*Trade-off between speed and noise margin.*


During pull-up, need:

- high current for fast switching,
- but also high resistance for high noise margin.


$\Rightarrow$  use *current source* as pull-up.

## 2. NMOS inverter with current-source pull-up


I-V characteristics of current source:

 

Equivalent circuit models:

 



large-signal model

 

small-signal model

- high current throughout voltage range:  $i_{SUP} \simeq I_{SUP}$
- high small-signal resistance,  $r_{oc}$ .

  NMOS inverter with current-source pull-up:















  Small-signal equivalent circuit model at  $V_M$ :




$$A_v = -g_{mn}(r_{on} // r_{op})$$

NMOS inverter with current-source pull-up allows fast switching with high noise margins.

But... when  $V_{IN} = V_{DD}$ , there is a direct current path between supply and ground

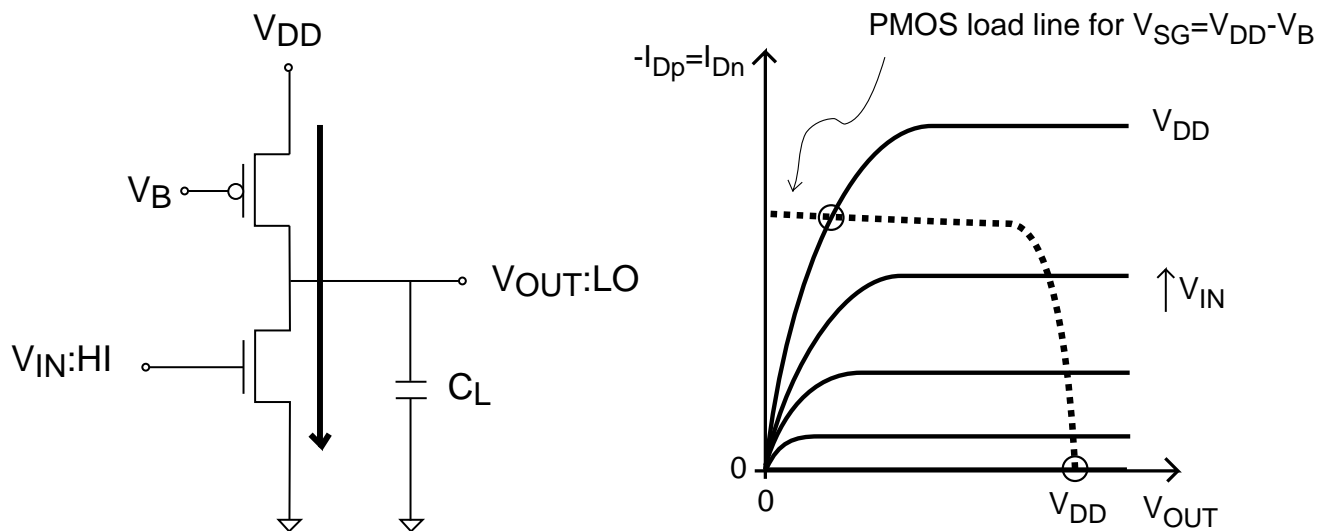
$\Rightarrow$  power consumption even if inverter is idling.



Would like to have current source that is *itself* switchable, *i.e.*, it shuts off when input is high  $\Rightarrow$  CMOS!

### 3. Complementary MOS (CMOS) Inverter

Circuit schematic:

 

Basic operation:

- $V_{IN} = 0 \Rightarrow V_{OUT} = V_{DD}$

$$V_{GSn} = 0 < V_{Tn} \Rightarrow \text{NMOS OFF}$$

$$V_{SGp} = V_{DD} > -V_{Tp} \Rightarrow \text{PMOS ON}$$

- $V_{IN} = V_{DD} \Rightarrow V_{OUT} = 0$

$$V_{GSn} = V_{DD} > V_{Tn} \Rightarrow \text{NMOS ON}$$

$$V_{SGp} = 0 < -V_{Tp} \Rightarrow \text{PMOS OFF}$$

No power consumption while idling in any logic state.

## Key conclusions

- In NMOS inverter with resistor pull-up: trade-off between noise margin and speed.
- Trade-off resolved using current-source pull-up: use PMOS as current source.
- In NMOS inverter with current-source pull-up: if  $V_{IN} = HI$ , power consumption even if inverter is idling.
- Complementary MOS: NMOS and PMOS switch alternatively  $\Rightarrow$  no power consumption while idling.