



# Chapter 5

## TWO-PORT NETWORKS

# Introduction

- Two-port networks have two ports or two pairs of terminals of interest.
- Two-port analysis allows us to focus on the relationships between the voltage and current variables of the two ports.
- Thus, it allows us to collapse the many equations of nodal and mesh to a single pair of equations.

## Introduction cont'd

- In other words the two-port network is treated as a black box modelled by the relationships between the four variables.
- The relationships between the two voltages and the two currents are described in terms of quantities known as parameters.
- The popular two-port parameters are admittance, impedance, hybrid and transmission.

## Introduction cont'd

- Knowing the two-port parameters of a network or system permits us to describe its operation when it is connected into a larger network (System Analysis).
- Two-port networks are used to model devices in electronics such as transistors and op-amps and electrical components such as transformers and transmission lines.

# Two-port network

- It has **input** (on the left) and **output** (on the right) ports for external connection.
- Each port is assumed to satisfy the port condition (i.e. **the current into the network at one terminal of a port is equal to the current flowing out the other terminal of the port** or **KCL must be satisfied at each port**).
- See next slide for the diagram.
- It is customary to label the voltages and currents as shown.

a


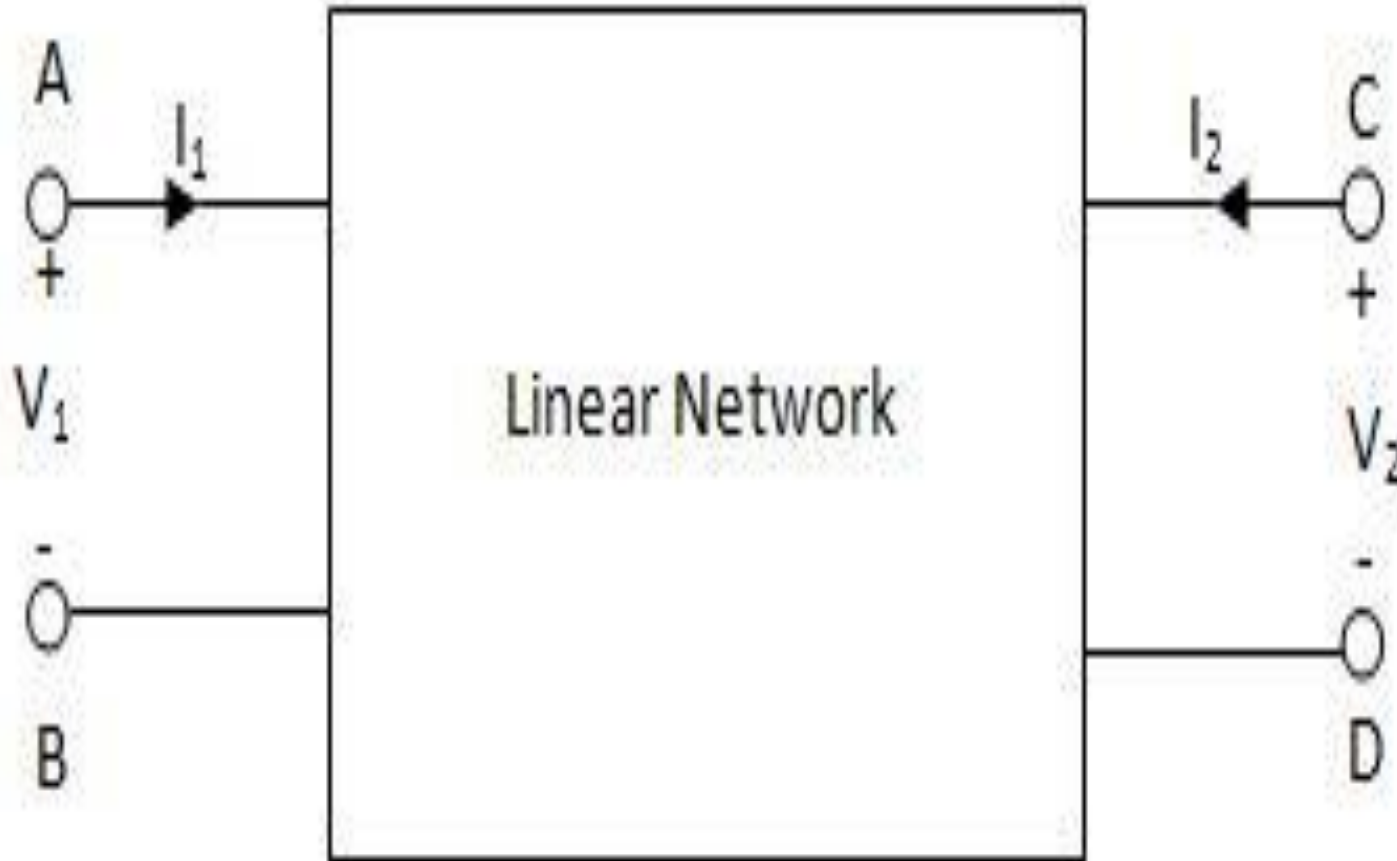


Diagram of Two-Port Network

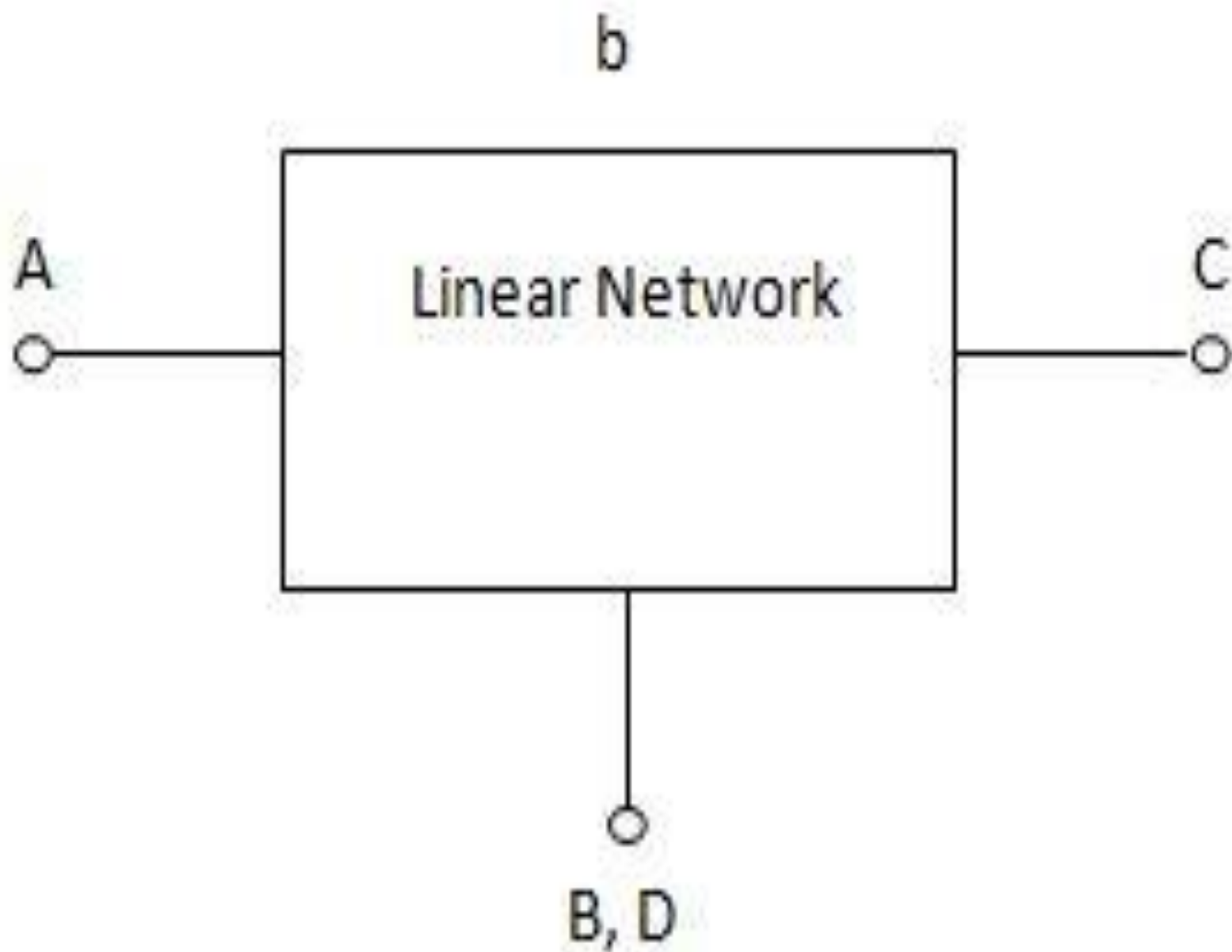- For some devices the two-port configuration may appear as 3-terminal device having one terminal common to both the input and output . See the next slide.
- The network consists of R, L and C elements, transformers, op – amps, dependent source but no independent sources.
- It is considered to be linear.





# Admittance Parameters (Y-parameters)

- Since the network is linear and contains no independent sources, the principle of superposition can be applied to determine the current,  $I_1$ .
- Applying this principle,  $I_1$  which is the sum of two components, one due to  $V_1$  and the other due to  $V_2$  is given by

$$I_1 = y_{11}V_1 + y_{12}V_2$$

- Similarly,  $I_2$  is given by

$$I_2 = y_{21}V_1 + y_{22}V_2$$

- Therefore, the two equations that describe the two-port network are:

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

- If the  $y$ -parameters are known, the input/output operation of the two-port is completely defined.

# Admittance parameters cont'd

- The y- parameters can be determined as follows:

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad (\text{short-circuit input admittance})$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad (\text{short-circuit transfer admittance})$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \quad (\text{short-circuit transfer admittance})$$


$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} \quad (\text{short-circuit output admittance})$$

## Admittance parameters cont'd


- As a group the  $y$ -parameters are referred to as the short-circuit admittance parameters.
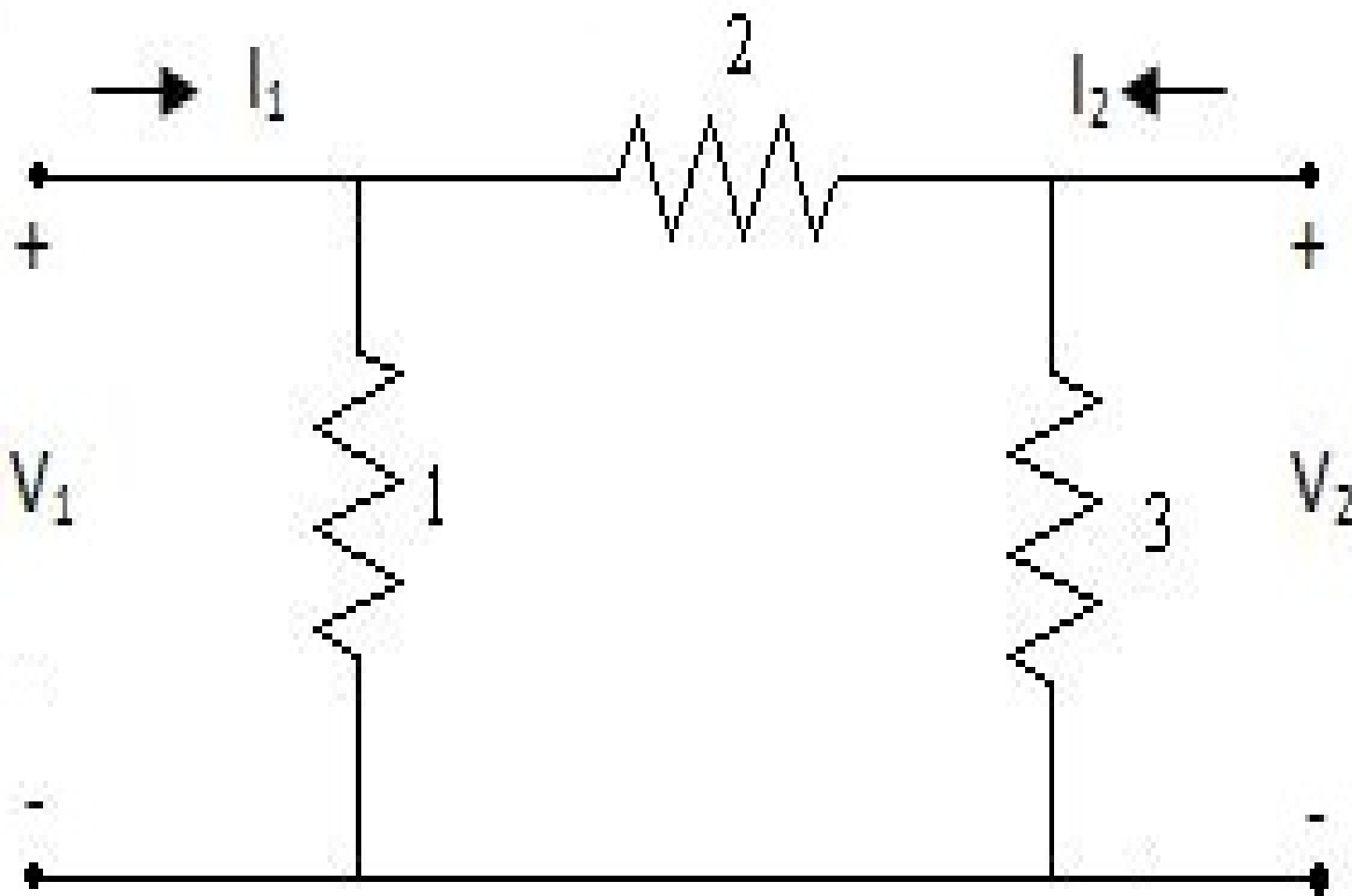
### Example 1

Determine the  $y$ -parameters for the two-port circuit shown on the next slide.




When the output is short-circuited:

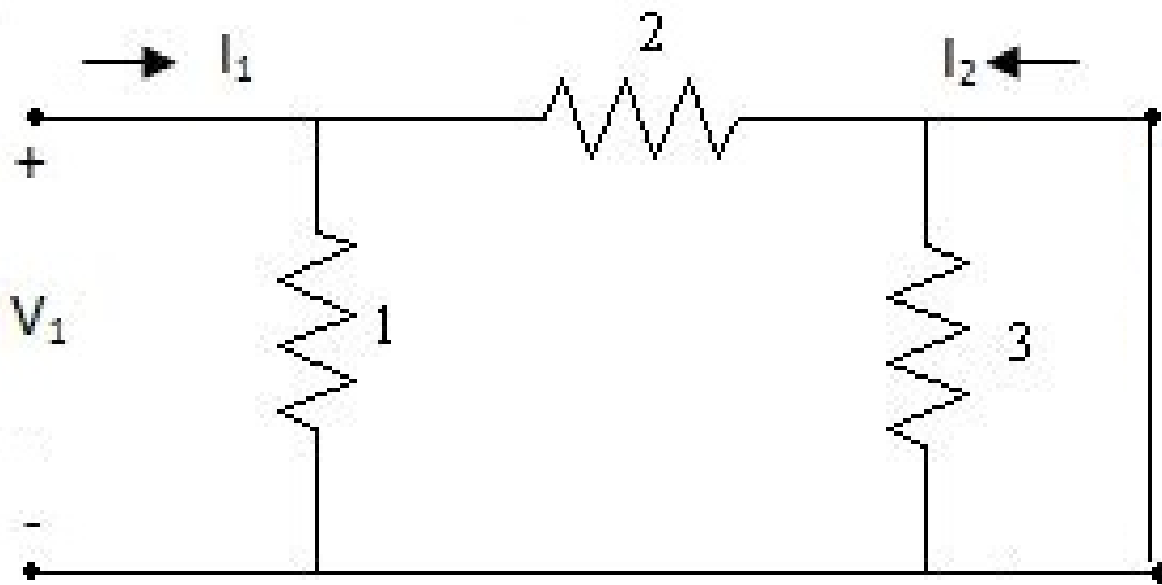

$$I_1 = \frac{V_1}{1} + \frac{V_1}{2} = V_1 \left( 1 + \frac{1}{2} \right) = \frac{3V_1}{2} \Rightarrow y_{11} = \frac{3}{2}S$$

$$I_2 = -\frac{V_1}{2} = \left( -\frac{1}{2} \right) V_1 \Rightarrow y_{21} = -\frac{1}{2}S$$

When the input is short-circuited:

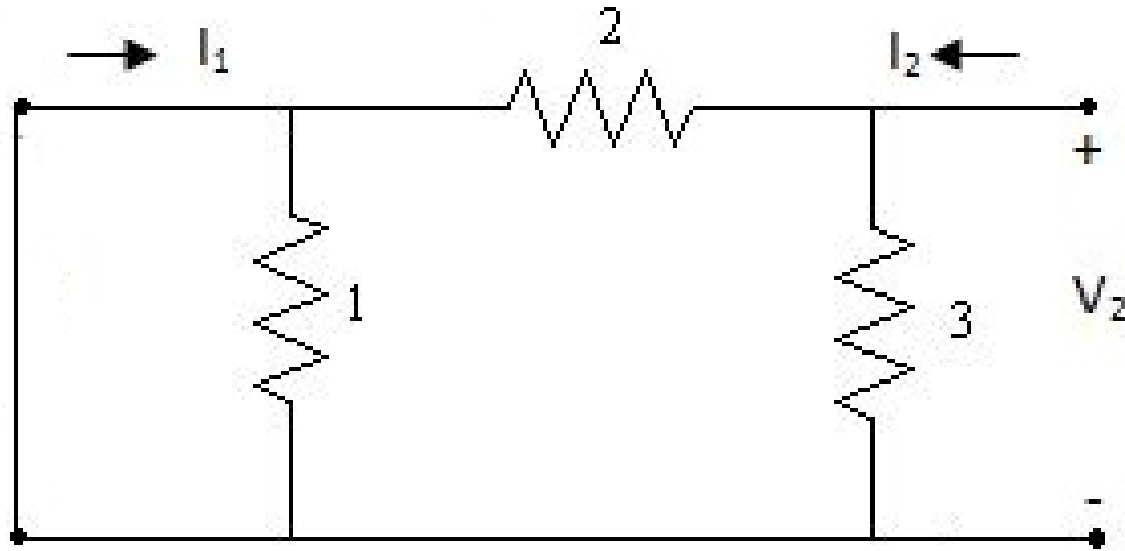

$$I_2 = \frac{V_2}{3} + \frac{V_2}{2} = V_2 \left( \frac{2}{6} + \frac{3}{6} \right) = \frac{5}{6} V_2 \Rightarrow y_{22} = \frac{5}{6} S$$

$$I_1 = -\frac{V_2}{2} \Rightarrow y_{12} = -\frac{1}{2} S$$


In the matrix form

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{3}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{5}{6} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



Note: Nodal analysis could have been used.



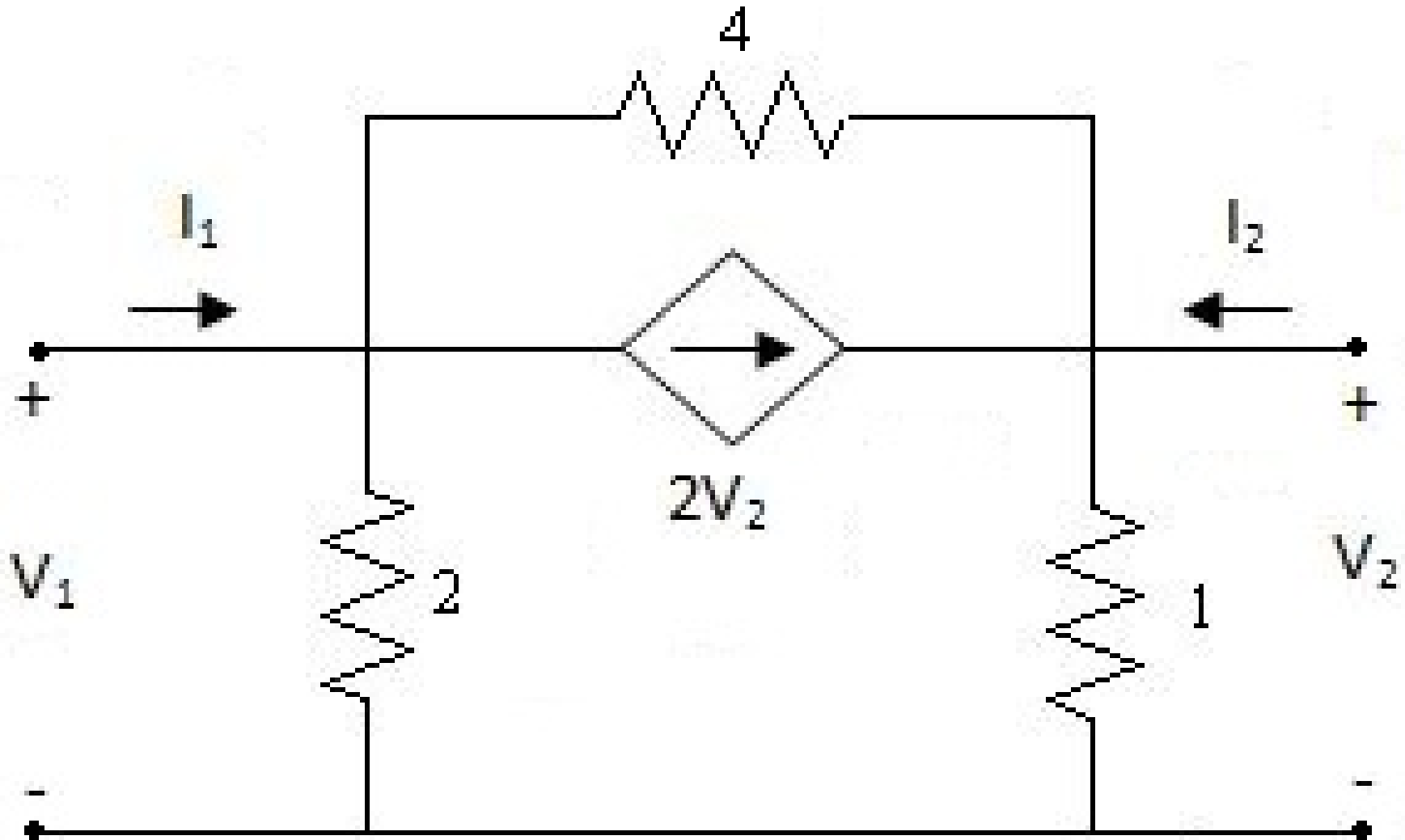**Example 2:** Find the y-parameters for the two-port circuit:



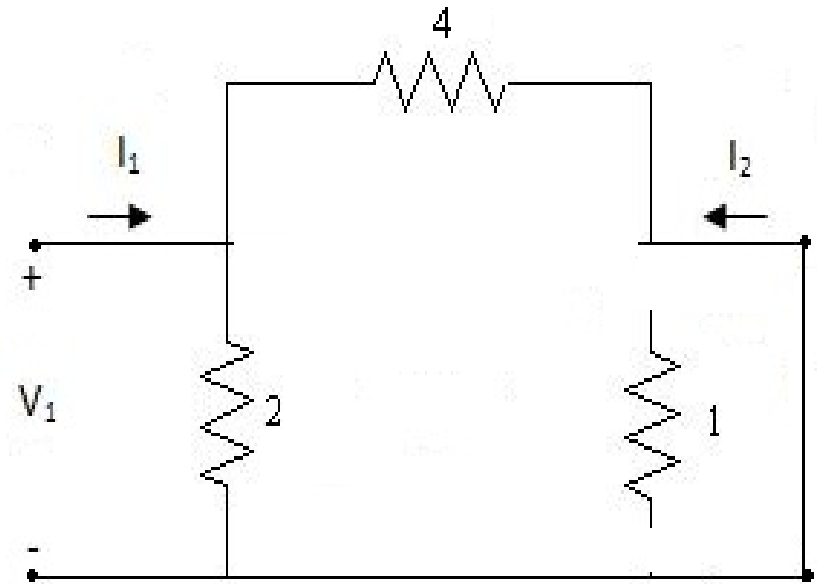
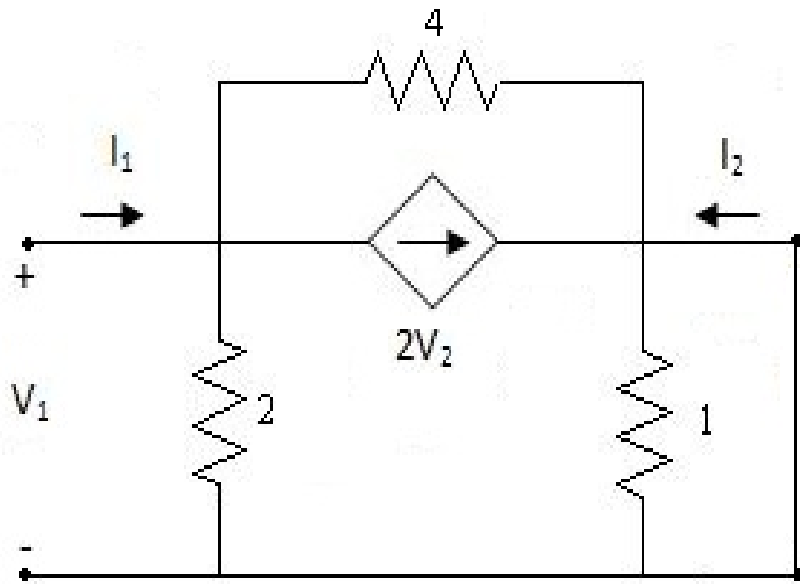
When the output is short-circuited, the controlled current source carries no current, i.e., that branch is open.



$$I_1 = \frac{V_1}{2} + \frac{V_1}{4} = \left(\frac{1}{2} + \frac{1}{4}\right) V_1 = \frac{3}{4} V_1 \Rightarrow y_{11} = \frac{3}{4}$$

$$I_2 = -\frac{V_1}{4} \Rightarrow y_{21} = -\frac{1}{4}$$

When the input is short-circuited:

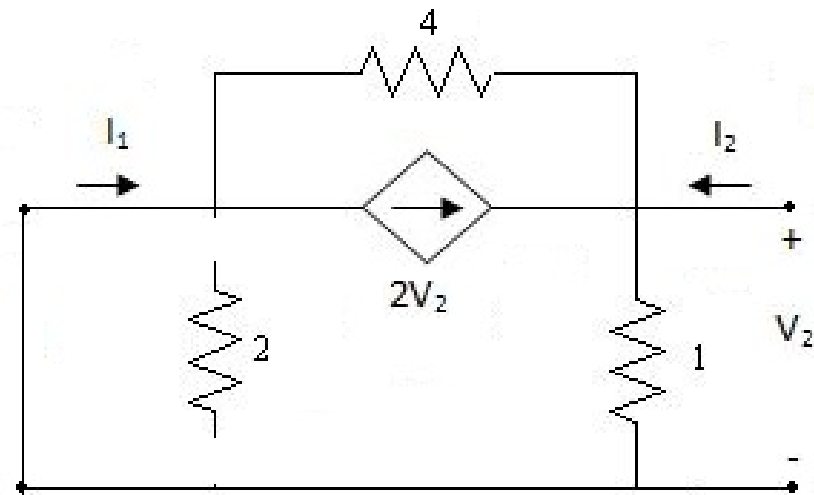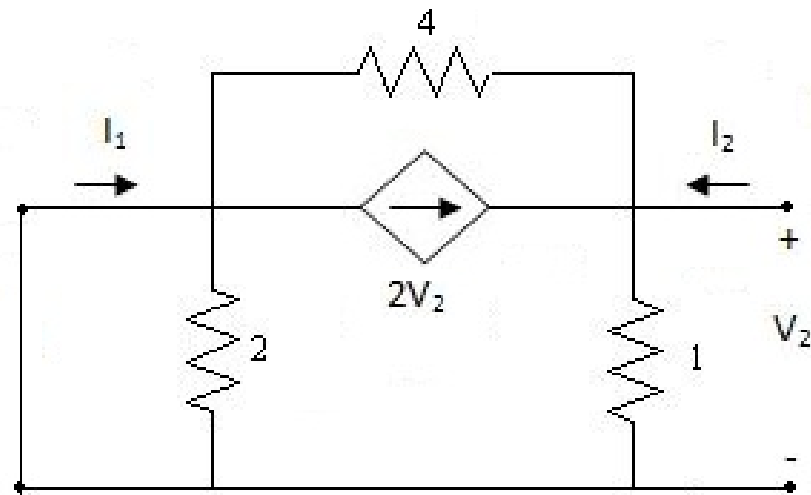

$$I_2 = \frac{V_2}{1} + \frac{V_2}{4} - 2V_2 = \left(1 + \frac{1}{4} - 2\right) V_2 = -\frac{3}{4} V_2 \Rightarrow y_{22} = -\frac{3}{4}$$

$$I_1 = -\frac{V_2}{4} + 2V_2 = \left(-\frac{1}{4} + 2\right) V_2 = \frac{7}{4} V_2 \Rightarrow y_{12} = -\frac{7}{4} S$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{3}{4} & \frac{7}{4} \\ -\frac{1}{4} & -\frac{3}{4} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

# Impedance Parameters (Z-parameters)

- By means of superposition, the input and output voltages can be expressed as the sum of two components, one due to  $I_1$  and the other due to  $I_2$ :

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

- The z- parameters can be derived as follows (See next slide):

The z- parameters can be derived as follows:

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad (\text{open-circuit input impedance})$$


$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad (\text{open-circuit transfer impedance})$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad (\text{open-circuit transfer impedance})$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \quad (\text{open-circuit output impedance})$$

The z-parameters are called open-circuit impedance parameters.

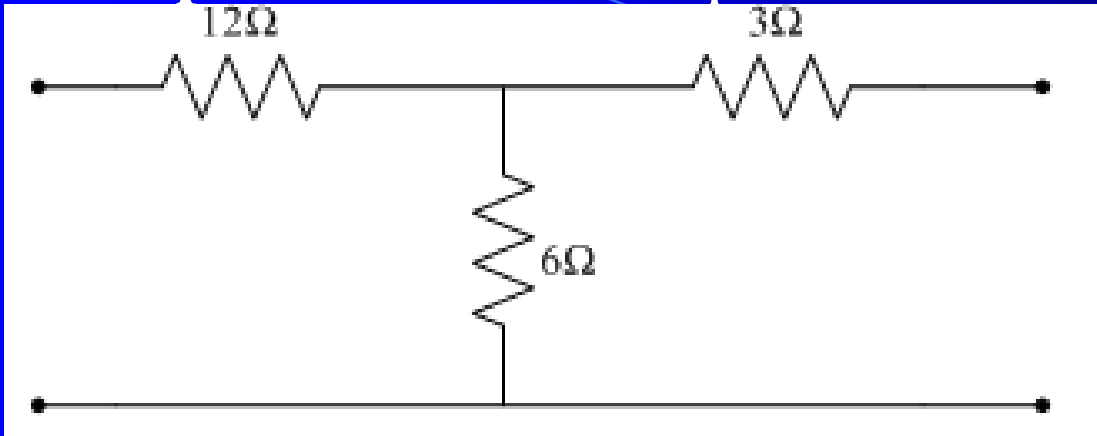● **Example 3:** Find the z-parameters for the network :



With the output open-circuited

$$Z_{11} = \frac{V_1}{I_1} = 12 + 6 = 18 \Omega \quad Z_{21} = \frac{V_2}{I_1} = \frac{6I_1}{I_1} = 6\Omega$$

With the input open-circuited

$$Z_{22} = \frac{V_2}{I_2} = 3 + 6 = 9 \Omega \quad Z_{12} = \frac{V_1}{I_2} = \frac{6I_2}{I_2} = 6 \Omega$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 18 & 6 \\ 6 & 9 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Verify using loop equations (or mesh equations)

# Hybrid Parameters (H-parameters)

- The parameters are known as hybrid because they have a mixture of units.
- They are used extensively to analyse transistor networks.
- The two-port equations are:

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

The parameters are determined as follows:

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2 = 0} \quad (\text{short-circuit input impedance})$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1 = 0} \quad (\text{open-circuit reverse voltage gain})$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2 = 0} \quad (\text{short-circuit forward current gain})$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1 = 0} \quad (\text{open-circuit output admittance})$$

In transistor network analysis, the parameters  $h_{11}$ ,  $h_{12}$ ,  $h_{21}$  and  $h_{22}$  are normally labelled  $h_i$ ,  $h_r$ ,  $h_f$  and  $h_o$ .



# Inverse Hybrid Parameters (g-parameters)

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$g_{11}$  = Open-circuit input admittance

$g_{12}$  = Short-circuit reverse current gain

$g_{21}$  = Open-circuit forward voltage gain

$g_{22}$  = Short-circuit output impedance