



COE 272

Digital Systems

Combinational Circuits Pt.2
(De/Multiplexers and En/Decoders)





Multiplexer

- A multiplexer is a special type of combinational circuit.
- It selects one out of n data inputs and routes it to the output
- To select n inputs, we require m select lines such that $2^m = n$.
- Depending on the digital code applied at the select inputs, one out of the n data sources is selected and transmitted to the single output Y .



Multiplexer

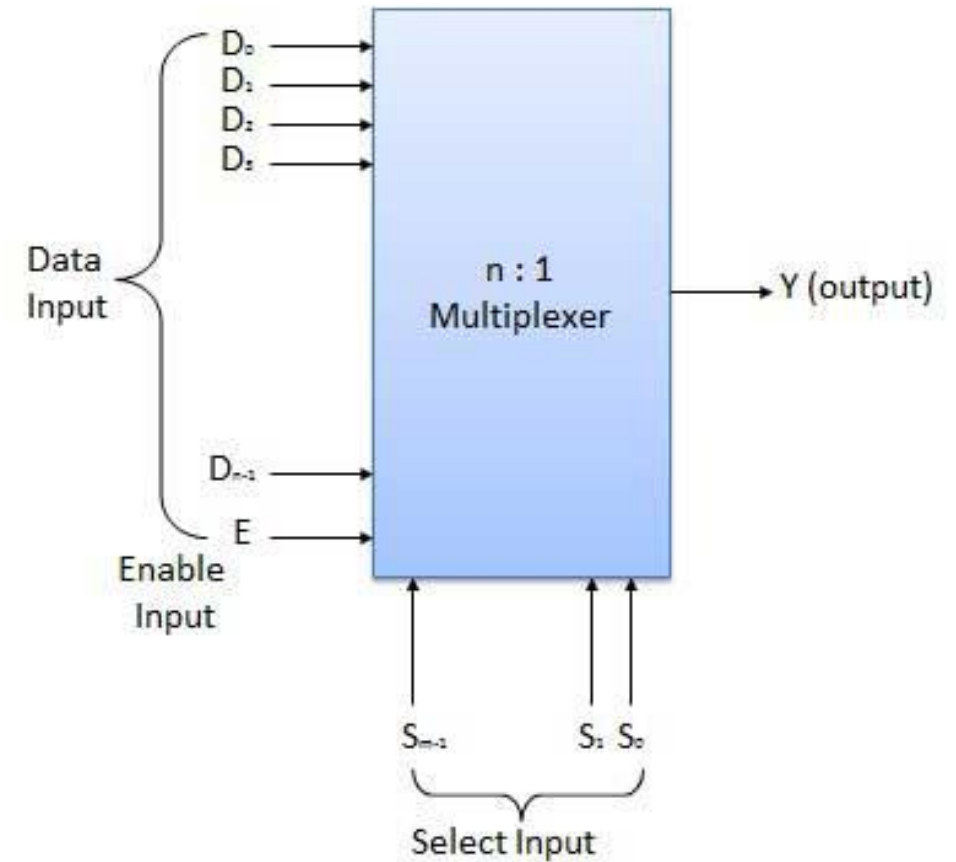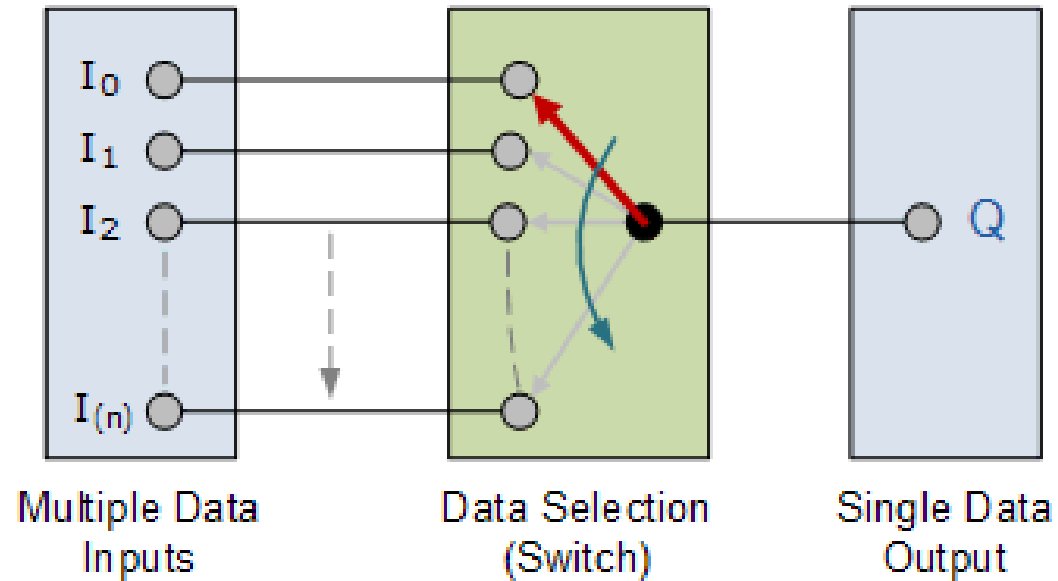



Necessity of multiplexers

- Mostly found in electronic systems, digital data is available on more than one line.
- It is essential to route this data over a single line
- Under such circumstances a circuit is needed to implement this function; the multiplexer is such a circuit.
- Multiplexers improve reliability of digital systems because it reduces the number of external wired connections




Advantages of multiplexers

- The use of multiplexers provide the following advantages:
 - It reduces the number of wires
 - Reduces the circuit complexity and cost
 - It simplifies the logic design
 - It does not need K-Maps and simplification



Typical application of MUX

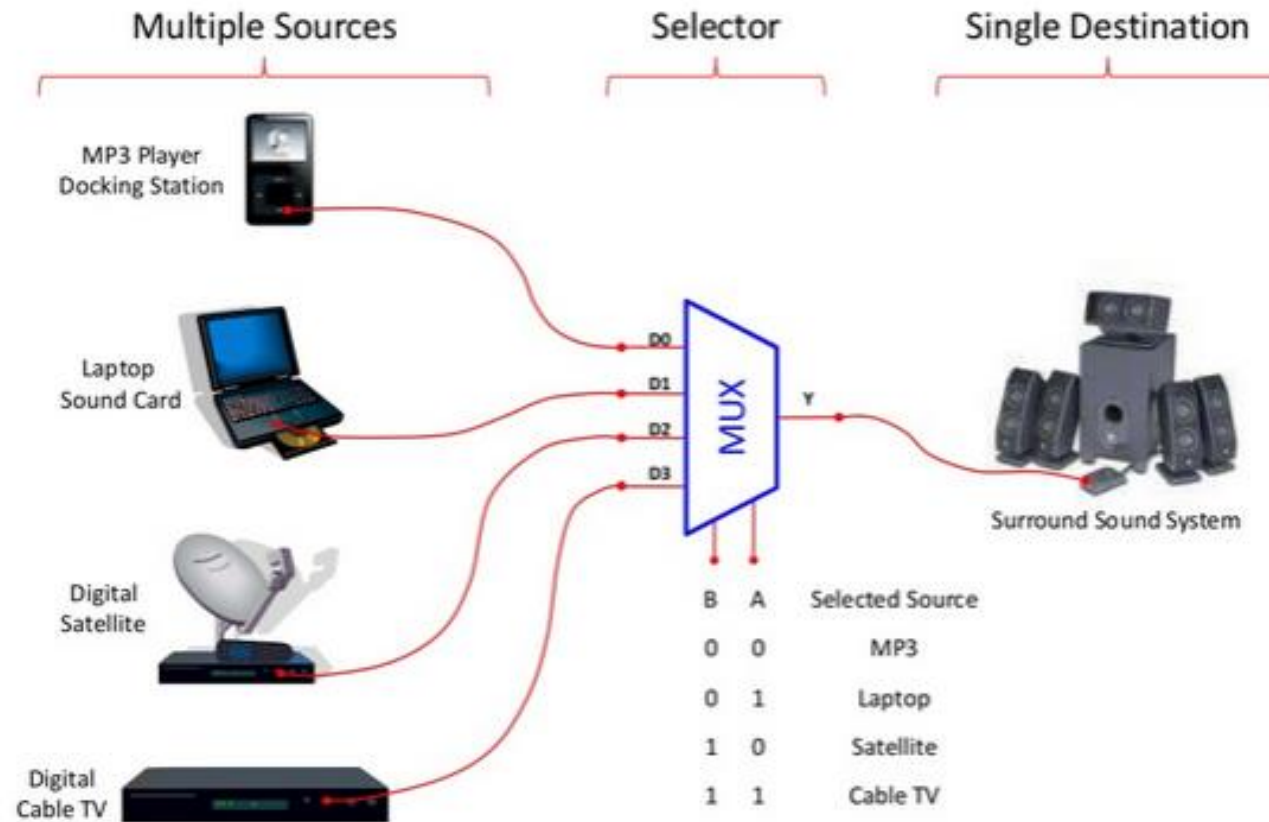




Classification of multiplexers

- Multiplexers are classified as under:
 - 2 : 1 multiplexer
 - 4 : 1 multiplexer
 - 8 : 1 multiplexer
 - 16 : 1 multiplexer



 2 : 1 multiplexer

- It has two data inputs D_0 and D_1 .
- It has one select input S , an enable input and one output



Enable	Select i/p (S)	Output Y
0	X	0
1	0	D_0
1	1	D_1

Truth table for 2 : 1 Mux



2 : 1 multiplexer

Enable E	Select S	D ₁	D ₀	Output Y
0	X	X	X	0
1	0	X	0	0
1	0	X	1	1
1	1	0	X	0
1	1	1	X	1


← $Y = ES'D_0$

← $Y = ESD_1$

$$Y = ES'D_0 + ESD_1$$




2 : 1 multiplexer

 



 4 : 1 multiplexer

- It has four data input lines, two select lines and one output line






4 : 1 multiplexer

Select Inputs		Output
S1	S0	
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃



4 : 1 multiplexer

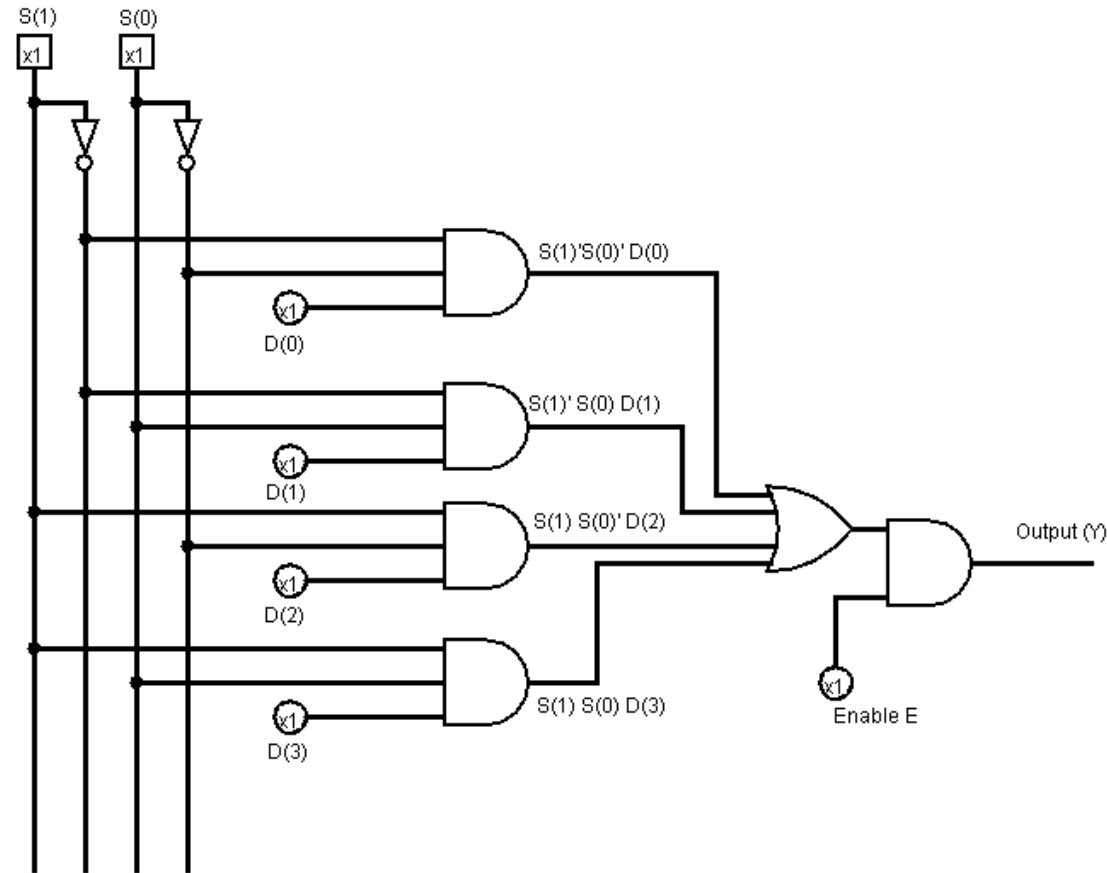


$$Y = \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_1 S_0 D_1 + S_1 \bar{S}_0 D_2 + S_1 S_0 D_3$$



 8 : 1 multiplexer

- It has eight data inputs, one enable input, three select inputs and one output






8 : 1 multiplexer

Enable E	Select Inputs			Output (Y) Y
	S2	S1	S0	
0	X	X	X	0
1	0	0	0	D ₀
1	0	0	1	D ₁
1	0	1	0	D ₂
1	0	1	1	D ₃
1	1	0	0	D ₄
1	1	0	1	D ₅
1	1	1	0	D ₆
1	1	1	1	D ₇




8 : 1 multiplexer

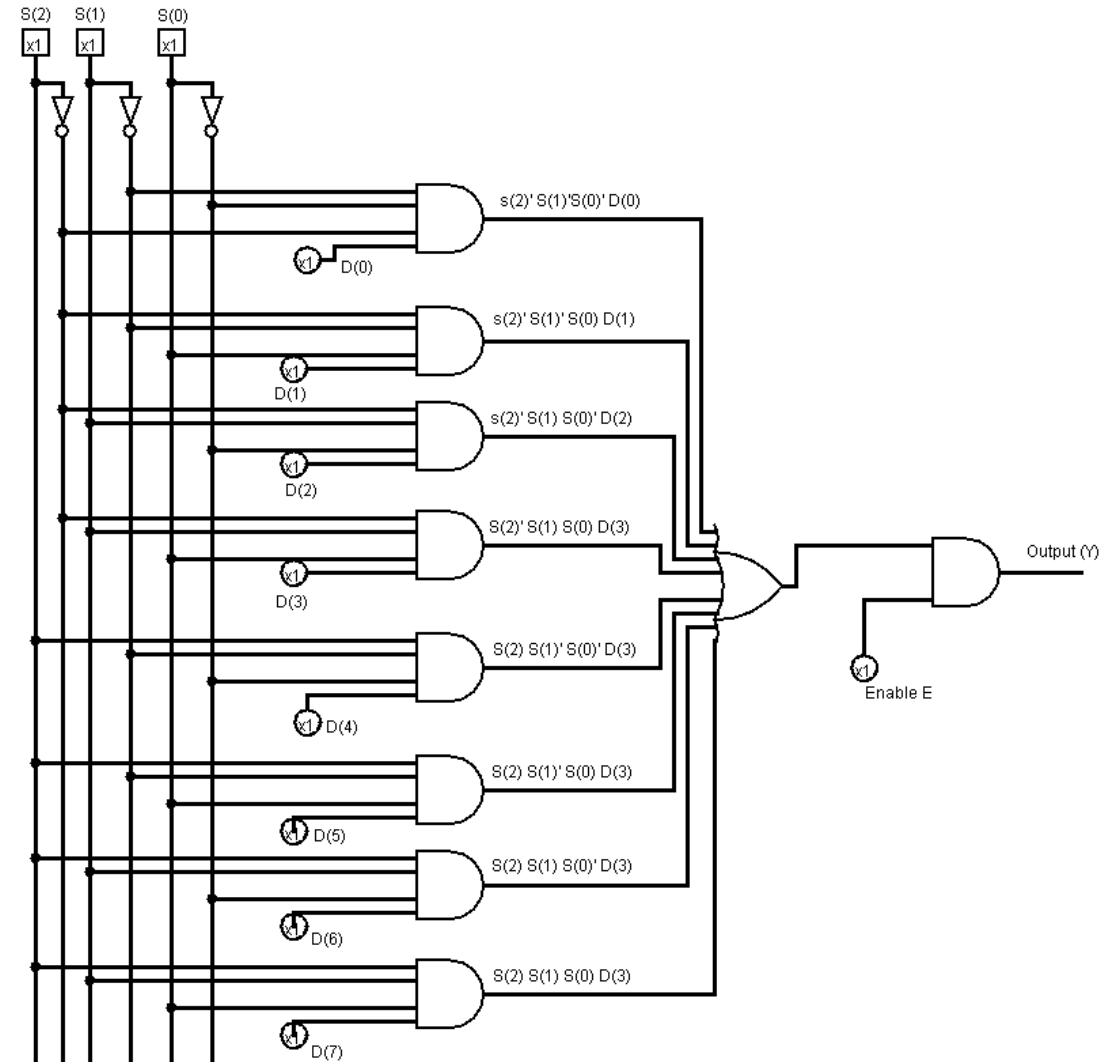



 16 : 1 multiplexer

- When the enable input is 0 the multiplexer outputs a 0
- When $E = 1$, we can select one of the 16 inputs with the help of the select input lines





16 : 1 multiplexer

Enable E	Select Input				Output Y
	S3	S2	S1	S0	
0	0	0	0	0	D0
1	0	0	0	1	D1
1	0	0	1	0	D2
1	0	0	1	1	D3
1	0	1	0	0	D4
1	0	1	0	1	D5
1	0	1	1	0	D6
1	0	1	1	1	D7
1	1	0	0	0	D8
1	1	0	0	1	D9
1	1	0	1	0	D10
1	1	0	1	1	D11
1	1	1	0	0	D12
1	1	1	0	1	D13
1	1	1	1	0	D14
1	1	1	1	1	D15



Applications of multiplexers

- The following are some application areas of MUX
 - It can be used as a data selector to select one out of many inputs
 - It can be used for simplification of logic design
 - In designing combinational circuits
 - In D/A converters
 - To minimize number of connections




Multiplexer Tree

- Multiplexers having more number of inputs can be obtained by cascading two or more MUX with less number of inputs.
- This phenomenon is known as **multiplexer tree**



Example

- Obtain an 8 : 1 MUX using 4 : 1 MUX

 

Select Lines			Output Y
S ₂	S ₁	S ₀	
0	0	0	D ₀
0	0	1	D ₁
0	1	0	D ₂
0	1	1	D ₃
1	0	0	D ₄
1	0	1	D ₅
1	1	0	D ₆
1	1	1	D ₇



Practice Example

- Implement a 4 : 1 MUX using 2 : 1 MUX
- Obtain an 16 : 1 MUX using 4 : 1 MUX
- Obtain an 16 : 1 MUX using 8 : 1 MUX
- Draw a 32 : 1 MUX tree using 4 : 1 MUX



Combinational Logic using MUX

- The design procedure is as follows:
 - First, identify the decimal number corresponding to each minterm/maxterm in the expression
 - The input lines of the MUX, corresponding to these numbers are connected to logic 1 level.
 - All other inputs of the MUX are connected to logic 0 level.
 - The input (literals) are connected to the select inputs.




Example

- Implement the following expression using a MUX:
 - $F(A, B, C) = \sum m(0, 2, 4, 6)$



Solution

 




Demultiplexers

- Demultiplexers are used at the other end of the data path to separate signals that are sharing a data path and distribute them to their respective destinations
 - *A demultiplexer performs the reverse operation of a multiplexer*
- At a time, only one output line is selected by the select lines and the input is transmitted to the select output line.
- The Enable (E) enables the demultiplexer




DEMUX

 



Typical Application of a DEMUX

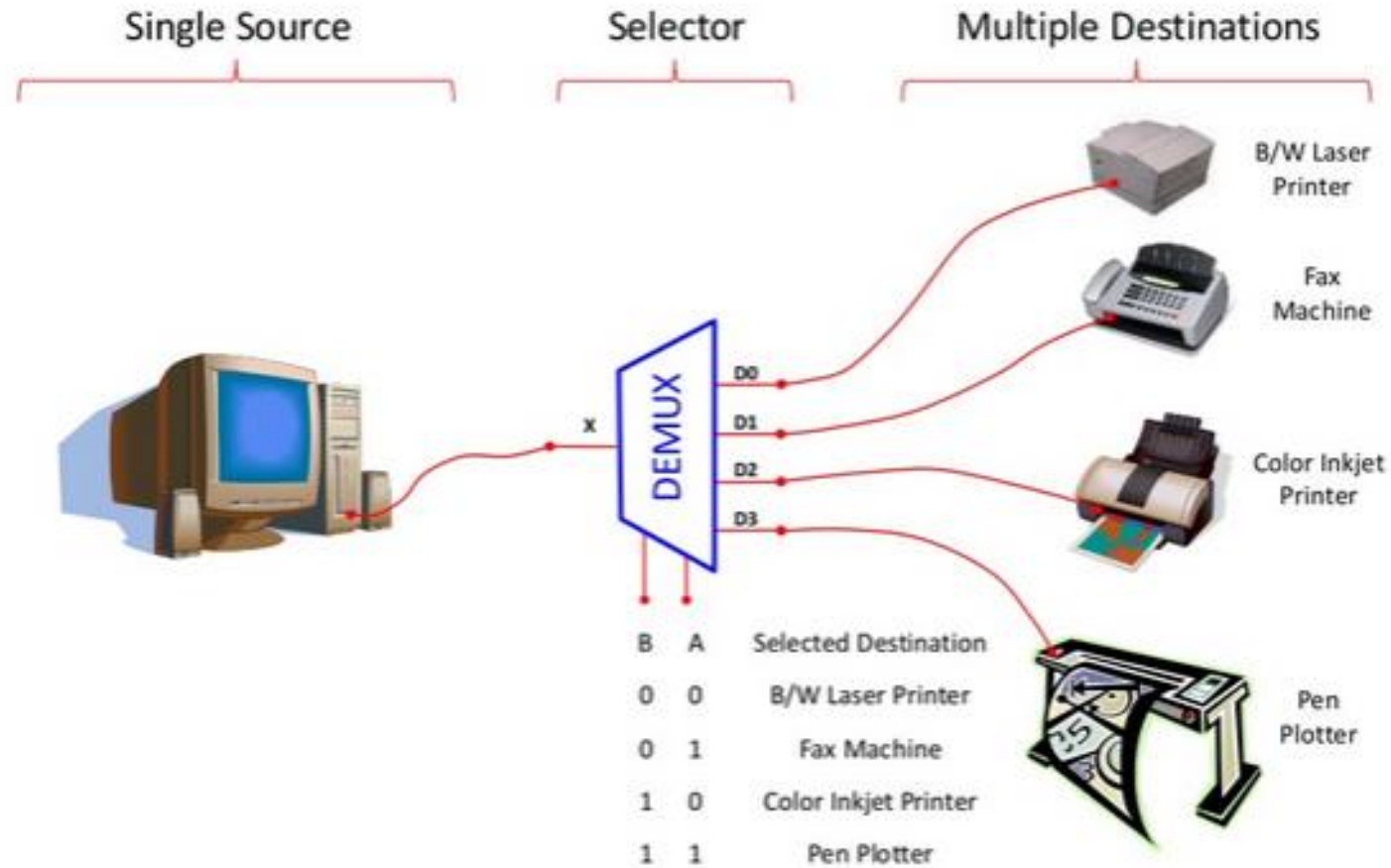



Classification of Demultiplexers

- 1 : 2 demultiplexer
- 1 : 4 demultiplexer
- 1 : 8 demultiplexer
- 1 : 16 demultiplexer



1 : 2 demultiplexer

- It has one data input Din, one select output So, one enable (E) input, and two outputs Y0 and Y1

Enable E	Select So	Output Y1 Y2	
0	X	0	0
1	0	0	Din
1	1	Din	0



1 : 2 demultiplexer


- Realization of 1 : 2 DEMUX

Enable E	Data D _{in}	Select S ₀	Output	
			Y ₁	Y ₀
0	X	X	0	0
1	0	0	0	0
1	1	0	0	1
1	0	1	0	0
1	1	1	1	0

Truth table for 1 : 2 demux




1 : 2 demultiplexer

 



1 : 4 demultiplexer

 



1 : 4 demultiplexer


- Realization of a 1 : 4 demultiplexer

E	Din	Select		Output				
E	Din	S1	S0	Y0	Y1	Y2	Y3	
1	0	0	0	0	0	0	0	Y0 is connected to Din
1	1	0	0	1	0	0	0	
1	0	0	1	0	0	0	0	Y1 is connected to Din
1	1	0	1	0	1	0	0	
1	0	1	0	0	0	0	0	Y2 is connected to Din
1	1	1	0	0	0	1	0	
1	0	1	1	0	0	0	0	Y3 is connected to Din
1	1	1	1	0	0	0	1	

Truth table for 1 : 4 demux



1 : 4 demultiplexer

 



1 : 8 demultiplexer

- It has one data input, eight data output, three select inputs and an enable input E.




1 : 8 demultiplexer

Enable E	Select			Outputs							
	S2	S1	S0	Y7	Y6	Y5	Y4	Y3	Y2	Y1	Y0
0	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	Din
1	0	0	1	0	0	0	0	0	0	Din	0
1	0	1	0	0	0	0	0	0	Din	0	0
1	0	1	1	0	0	0	0	Din	0	0	0
1	1	0	0	0	0	0	Din	0	0	0	0
1	1	0	1	0	0	Din	0	0	0	0	0
1	1	1	0	0	Din	0	0	0	0	0	0
1	1	1	1	Din	0	0	0	0	0	0	0

Truth table for 1 : 8 demux



1 : 8 demultiplexer

 



1 : 16 demultiplexer

- It has one data input D_{in} , four select lines S_0, S_1, S_2, S_3 .
- It has sixteen outputs and one enable input



Exercise

- Write the truth table for the 1 : 16 DEMUX
- Implement the above truth table using logic gates



Demultiplexer Tree (Exercise)

- Obtain a 1 : 4 demultiplexer using 1 : 2 demultiplexer
- Obtain a 1 : 8 demultiplexer using two 1 : 4 demultiplexer
- Obtain a 1 : 32 demultiplexer using four 1 : 8 demultiplexer and one 1 : 4 demultiplexer



Performance Comparison between MUX and DEMUX

Parameter	Multiplexer	Demultiplexer
Type of Logic Circuit	Combinational	Combinational
Number of Data Inputs	n	1
Number of Select Inputs	m	m
Number of Data Output	1	n
Relation between input/output lines and select lines	$n = 2^m$	$n = 2^m$
Operation principle	Many to 1 or as data selector	1 to many or data distributor
Application	<ul style="list-style-type: none">As a universal logic circuit, i.e. we can implement any combinational circuit using a MUXIn time division multiplexing (TDM) at the sending end	<ul style="list-style-type: none">We can implement some combinational circuitIn TDM systems at the receiving end




Decoder

- A decoder is a combinational circuit
- It converts n-bit binary information at its input into a maximum of 2^n output lines.
 - E.g. if $n = 2$, then we can design up to a 2 : 4 decoder
- Decoders are widely used in the memory system of the computer where they respond to the address code generated by the central processor to activate a particular memory location




Decoder

 



2 to 4 Line Decoder

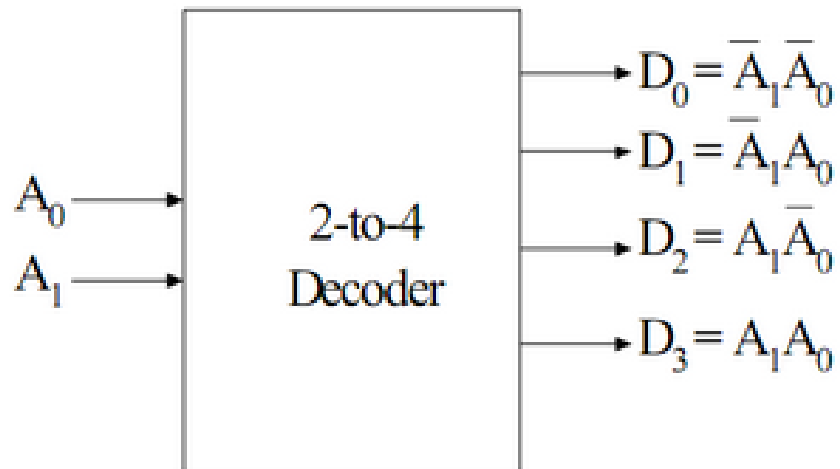
- There are two inputs (A_0 and A_1) and 4 outputs (D_0 , D_1 , D_2 , D_3).
- The truth table below explains the operation of the 2 to 4 line decoder



A_1	A_0	D_3	D_2	D_1	D_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0




2 to 4 Line Decoder

 



3 to 8 Line Decoder

 



3 to 8 Line Decoder

Dec. Code	Inputs			Outputs							
	A ₂	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
2	0	1	0	0	0	1	0	0	0	0	0
3	0	1	1	0	0	0	1	0	0	0	0
4	1	0	0	0	0	0	0	1	0	0	0
5	1	0	1	0	0	0	0	0	1	0	0
6	1	1	0	0	0	0	0	0	0	1	0
7	1	1	1	0	0	0	0	0	0	0	1



The diagram shows a 3-to-8 decoder implemented with three 3-input AND gates and three inverters. The inputs are A_0 , A_1 , and A_2 . Each input line is connected to all three AND gates. Additionally, each input line is connected to an inverter, and the output of each inverter is connected to all three AND gates. This configuration allows each AND gate to produce one of the eight possible minterms of the three inputs. The outputs are labeled as follows:

- $D_0 = \bar{A}_2 \bar{A}_1 \bar{A}_0$
- $D_1 = \bar{A}_2 \bar{A}_1 A_0$
- $D_2 = \bar{A}_2 A_1 \bar{A}_0$
- $D_3 = \bar{A}_2 A_1 A_0$
- $D_4 = A_2 \bar{A}_1 \bar{A}_0$
- $D_5 = A_2 \bar{A}_1 A_0$
- $D_6 = A_2 A_1 \bar{A}_0$
- $D_7 = A_2 A_1 A_0$




Decoder Expansion

- It is possible to build larger decoders using two or more smaller ones
 - A 6 –to- 64 decoder can be designed with four 4-to-16 decoders and one 2-to-4 decoder



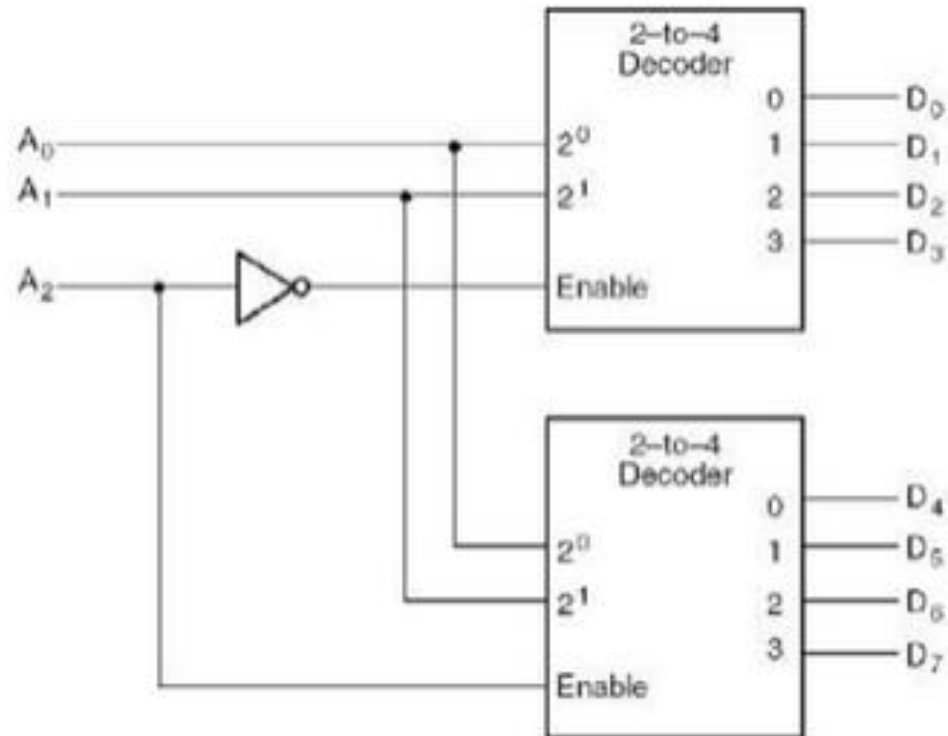Example

- Construct a 3-to-8 decoder using two 2-to-4 decoders with enable inputs





Combinational Circuit Implementation using Decoders

- A decoder provides the 2^n minterms of n input variables
- Since any Boolean functions can be expressed as a sum of minterms, one can use a decoder to implement any function of n variables.
- The decoder is used to generate the minterms and an additional OR gate is used to generate the sum of the required minterms
- In this way, any combinational circuit with n inputs and m outputs can be implemented using an n -to- 2^n decoder in addition to m OR gates

N/B: No simplification is required, because we need SSOP in order to work



Decoder Implementation of a Full Adder


Decimal value	Input			Output	
	X	Y	Z	S	C
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

$$S(X, Y, Z) = m(1, 2, 4, 7)$$

$$C(X, Y, Z) = m(3, 5, 6, 7)$$



Decoder Implementation of a Full Adder

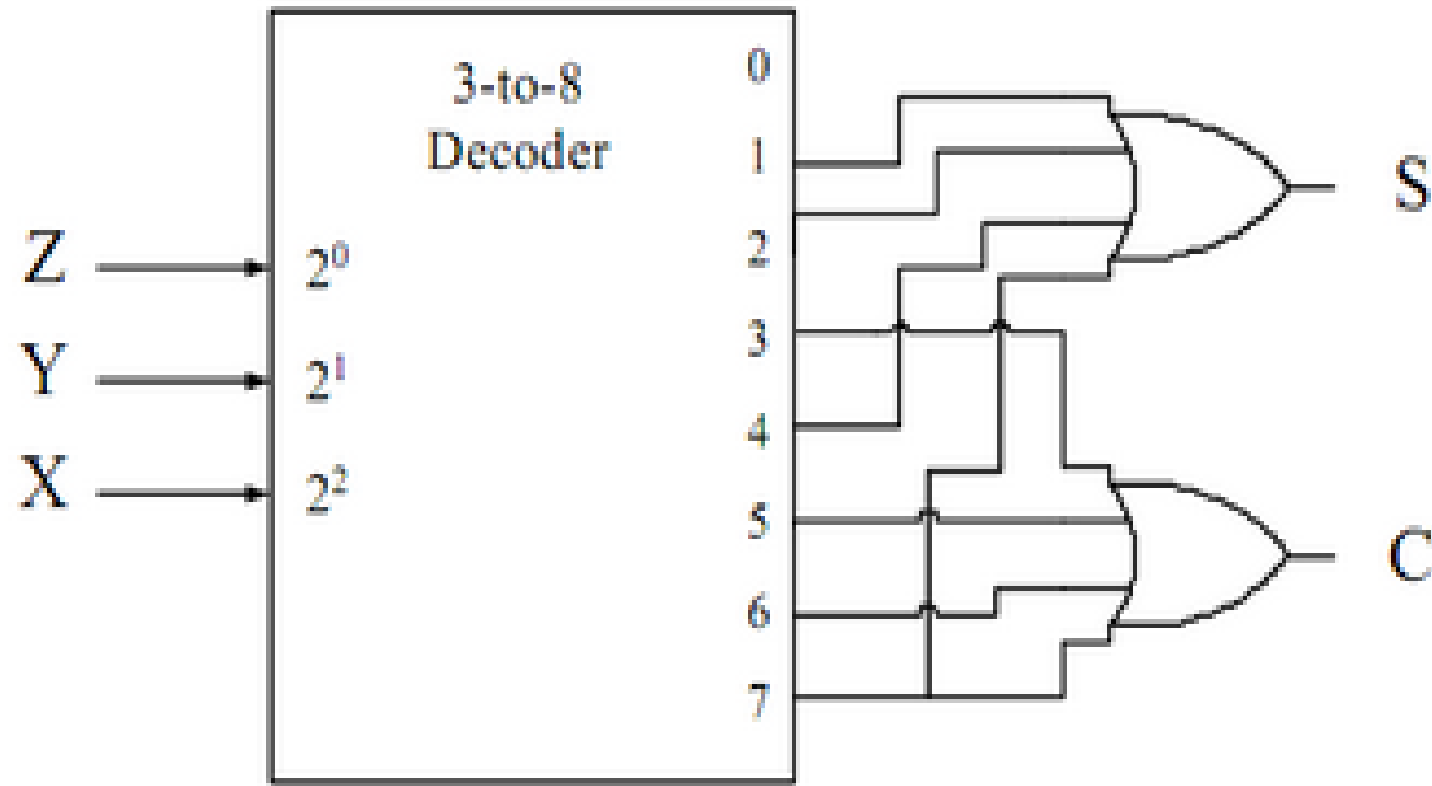



Practice Exercise

- Implement a 4 : 16 decoder using 3 : 8 decoders
- Implement a subtractor circuit using decoders




Encoders

- An encoder has
 - 2^n inputs
 - n outputs
- Its outputs the binary value of the selected (or active) input
- Performs the inverse operation of a decoder
- Issues
 - What if more than one input is active?
 - What if no inputs are active?



Encoders

 

Y_0	Y_1	Y_2	Y_3	A	B
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1



Classification of Encoders

- Priority Encoder
- Decimal to BCD Encoder
- Octal to Binary Encoder
- Hexadecimal to Binary Encoder




Priority Encoder

- If more than one input is active, the higher order input has priority over the lower-order input
 - The higher value is encoded on the output
- A valid indicator, d , is included to indicate whether or not the output is valid
 - Output is invalid when no inputs are active
 - $d = 0$
 - Output is valid when at least one input is active
 - $d = 1$



Priority Encoders

 

y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7	a	b	c	d
0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
X	1	0	0	0	0	0	0	0	0	1	1
X	X	1	0	0	0	0	0	0	1	0	1
X	X	X	1	0	0	0	0	0	1	1	1
X	X	X	X	1	0	0	0	1	0	0	1
X	X	X	X	X	1	0	0	1	0	1	1
X	X	X	X	X	X	1	0	1	1	0	1
X	X	X	X	X	X	X	1	1	1	1	1